


EEE 141 ELECTRICAL CIRCUITS

Dr. Shaikh Asif Mahmood
Associate professor, BUET

Adjunct Faculty, ECE, NSU



BASIC LAWS

Series Resistors and Voltage Division.

Parallel Resistors and Current Division.

Wye-Delta Transformations.

PARALLEL RESISTORS AND CURRENT DIVISION

Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.


The equivalent resistance of a circuit with N resistors in parallel is:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


The total current i is shared by the resistors in inverse proportion to their resistances. The current divider can be expressed as:

$$i_n = \frac{v}{R_n} = \frac{iR_{eq}}{R_n}$$

EXAMPLE

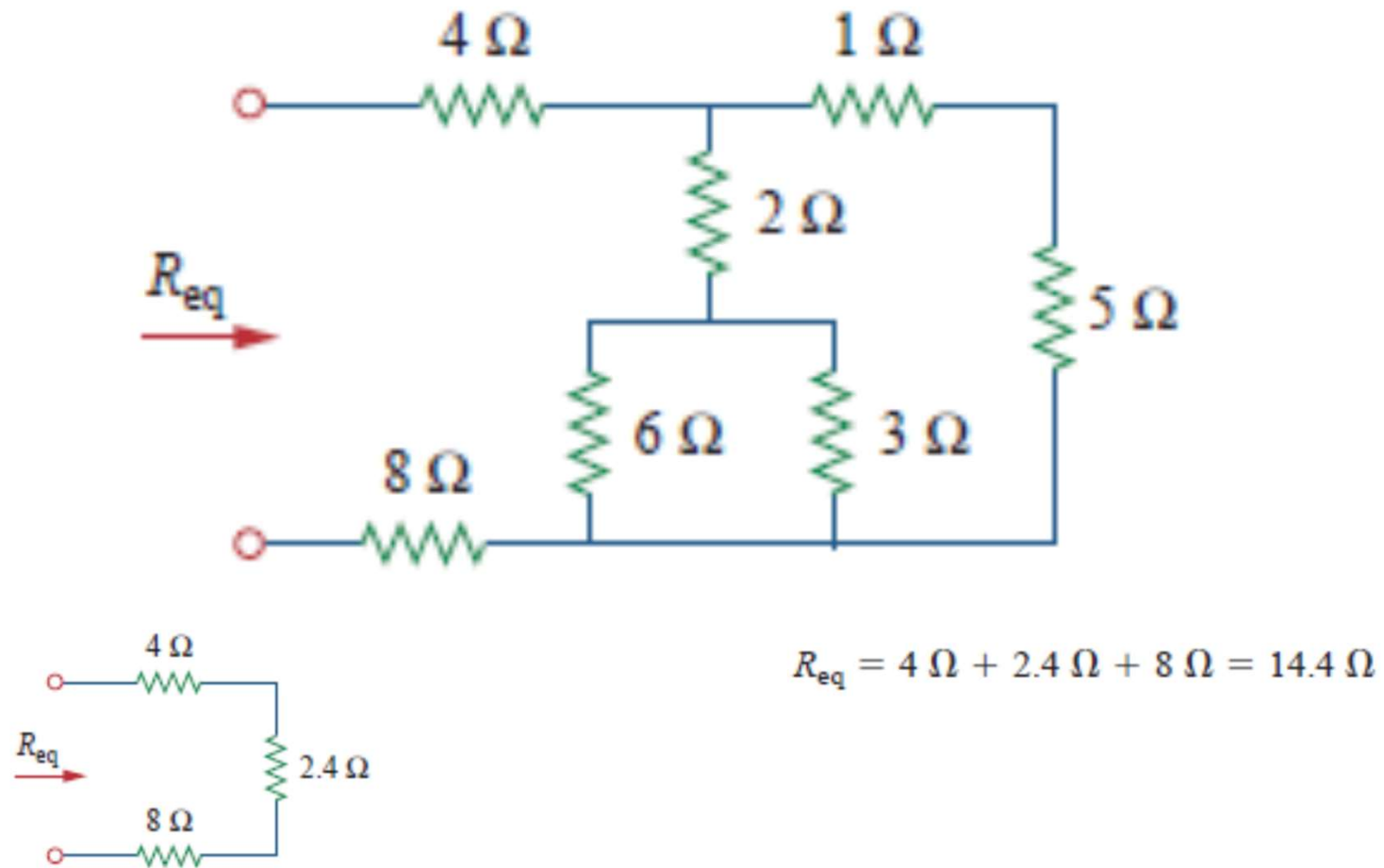

EXAMPLE

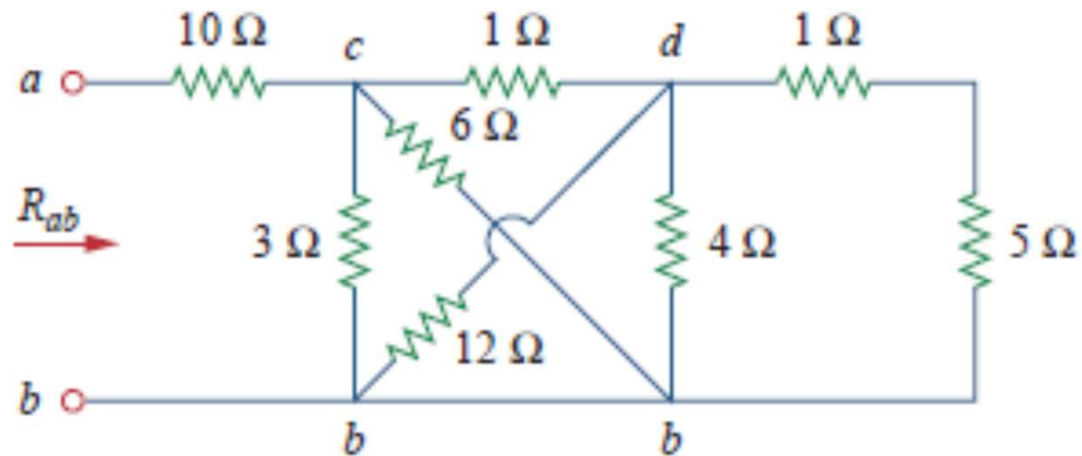

$$2 \Omega \parallel 3 \Omega = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$$

This 1.2- Ω resistor is in series with the 10- Ω resistor, so that

$$R_{ab} = 10 + 1.2 = 11.2 \Omega$$

EXAMPLE

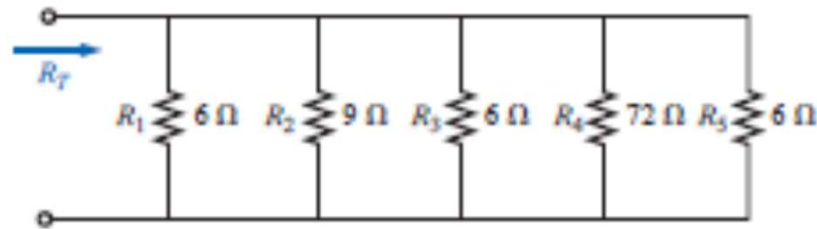


FIG. 6.13
Example 6.7.

Solution: The network is redrawn in Fig. 6.14:

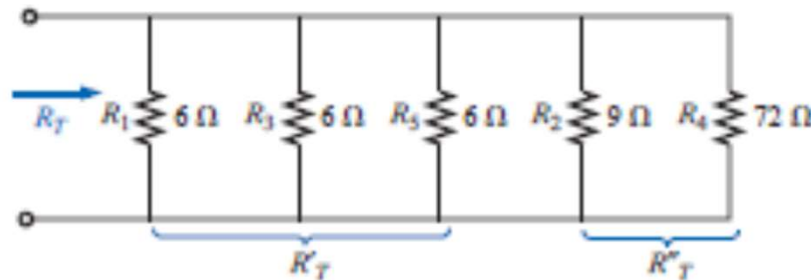


FIG. 6.14
Network of Fig. 6.13 redrawn.

$$R'_T = \frac{R}{N} = \frac{6 \Omega}{3} = 2 \Omega$$

$$R''_T = \frac{R_2 R_4}{R_2 + R_4} = \frac{(9 \Omega)(72 \Omega)}{9 \Omega + 72 \Omega} = \frac{648 \Omega}{81} = 8 \Omega$$

and

$$R_T = R'_T \parallel R''_T$$

↑ is parallel with

$$= \frac{R'_T R''_T}{R'_T + R''_T} = \frac{(2 \Omega)(8 \Omega)}{2 \Omega + 8 \Omega} = \frac{16 \Omega}{10} = 1.6 \Omega$$

EXAMPLE

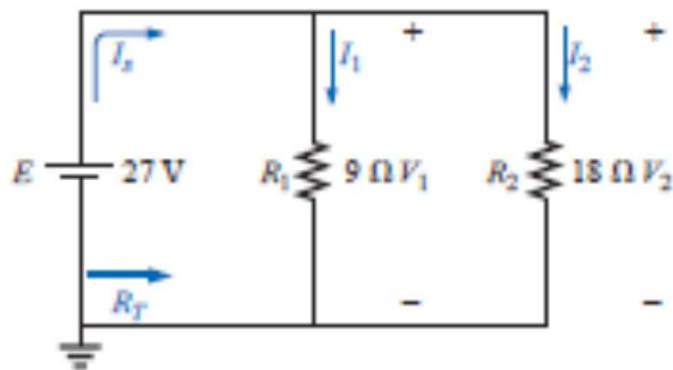


FIG. 6.22
Example 6.11.

EXAMPLE 6.11 For the parallel network of Fig. 6.22:

- Calculate R_T .
- Determine I_s .
- Calculate I_1 and I_2 , and demonstrate that $I_s = I_1 + I_2$.
- Determine the power to each resistive load.
- Determine the power delivered by the source, and compare it to the total power dissipated by the resistive elements.

Solutions:

$$\text{a. } R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9 \, \Omega)(18 \, \Omega)}{9 \, \Omega + 18 \, \Omega} = \frac{162 \, \Omega}{27} = 6 \, \Omega$$

EXAMPLE

EXAMPLE 6.12 Given the information provided in Fig. 6.23:

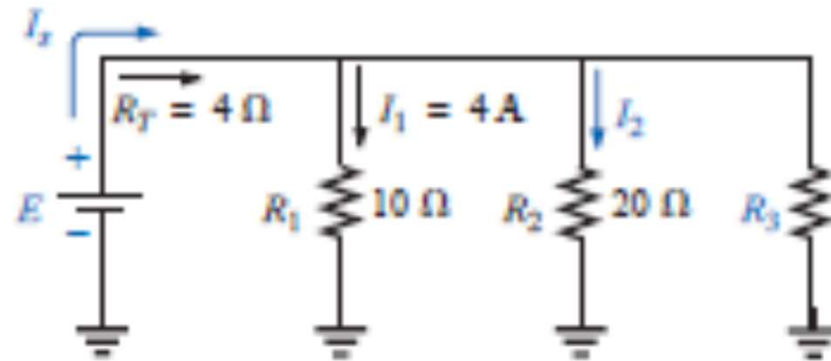


FIG. 6.23
Example 6.12.

- Determine R_3 .
- Calculate E .
- Find I_x .
- Find I_2 .
- Determine P_2 .

EXAMPLE

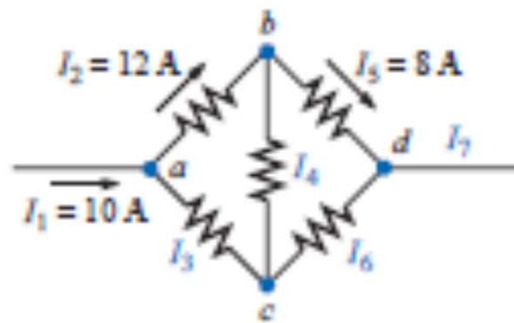


FIG. 6.30
Example 6.16.

EXAMPLE 6.16 Find the magnitude and direction of the currents I_3 , I_4 , I_6 , and I_7 for the network of Fig. 6.30. Even though the elements are not in series or parallel, Kirchhoff's current law can be applied to determine all the unknown currents.

Solution: Considering the overall system, we know that the current entering must equal that leaving. Therefore,

$$I_7 = I_1 = 10\text{ A}$$

Since 10 A are entering node a and 12 A are leaving, I_3 must be supplying current to the node.

CURRENT DIVIDER RULE

For the particular case of *two parallel resistors*, as shown in Fig. 6.34,

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

and

$$I_1 = \frac{R_T}{R_1} I = \frac{\frac{R_1 R_2}{R_1 + R_2}}{R_1} I$$

and

$$I_1 = \frac{R_2 I}{R_1 + R_2} \quad \text{Note difference in subscripts.} \quad (6.10)$$

Similarly for I_2 ,

$$I_2 = \frac{R_1 I}{R_1 + R_2} \quad (6.11)$$

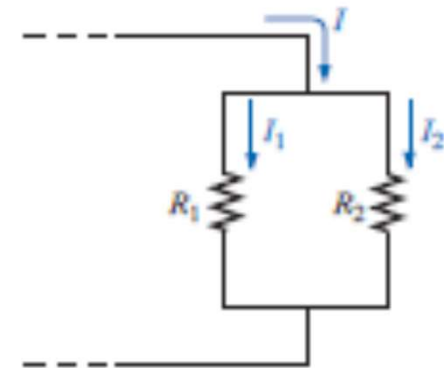


FIG. 6.34

Developing an equation for current division between two parallel resistors.

EXAMPLE

EXAMPLE 6.18 Find the current I_1 for the network of Fig. 6.36.


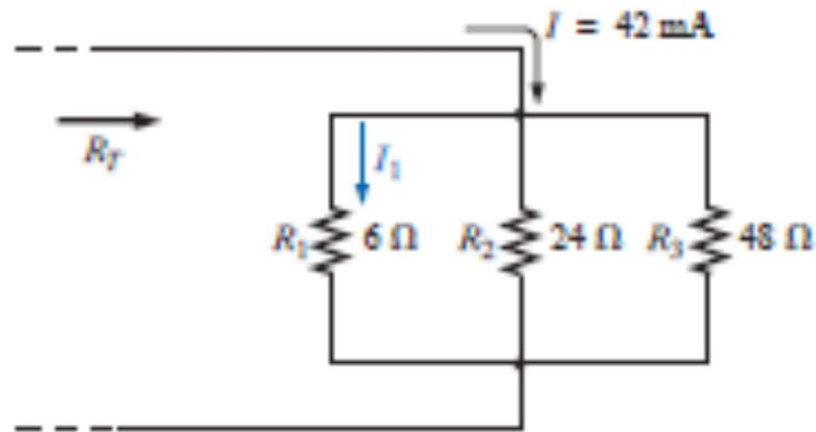


FIG. 6.36
Example 6.18


Solution: There are two options for solving this problem. The first is to use Eq. (6.9) as follows:

$$\begin{aligned}\frac{1}{R_T} &= \frac{1}{6\ \Omega} + \frac{1}{24\ \Omega} + \frac{1}{48\ \Omega} = 0.1667\ \text{S} + 0.0417\ \text{S} + 0.0208\ \text{S} \\ &= 0.2292\ \text{S}\end{aligned}$$


OPEN CIRCUIT

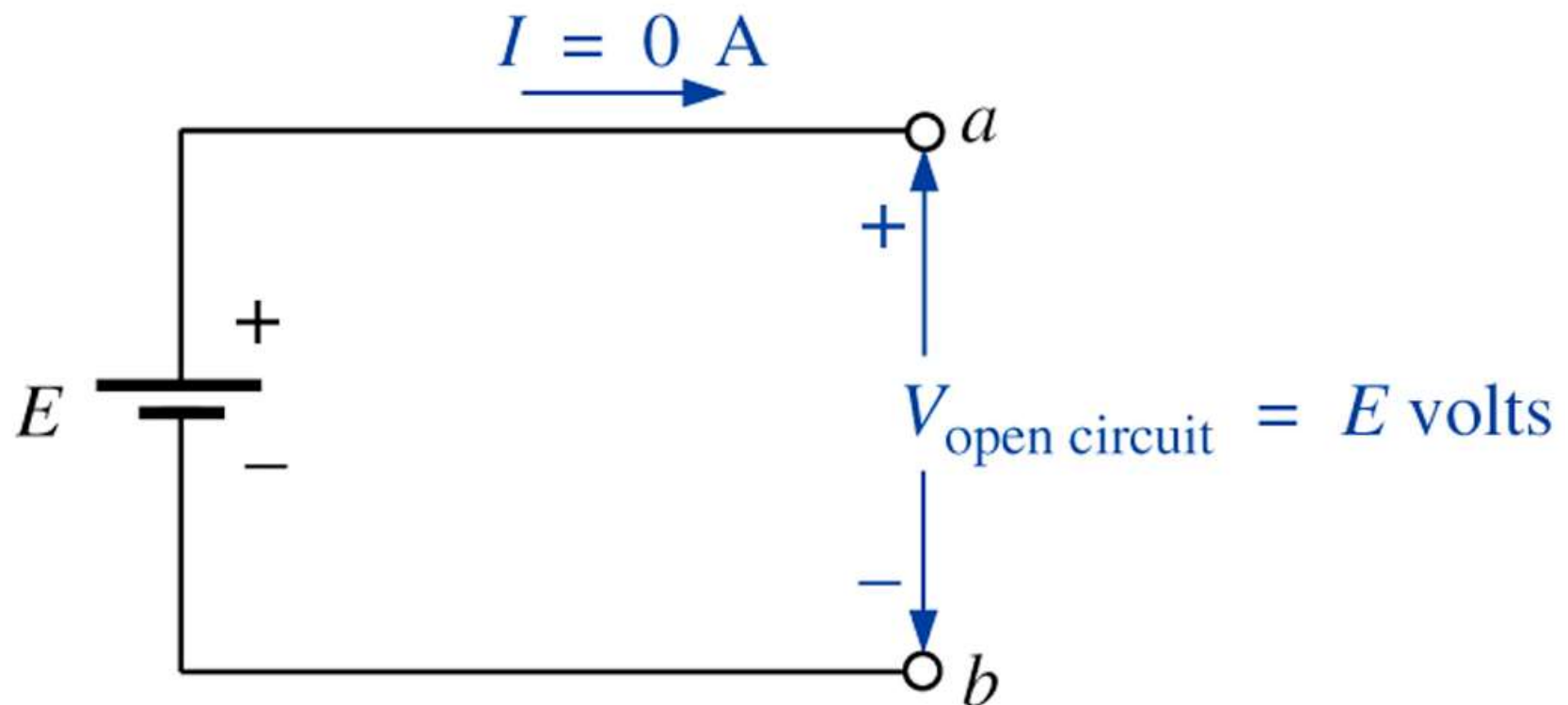

SHORT CIRCUIT

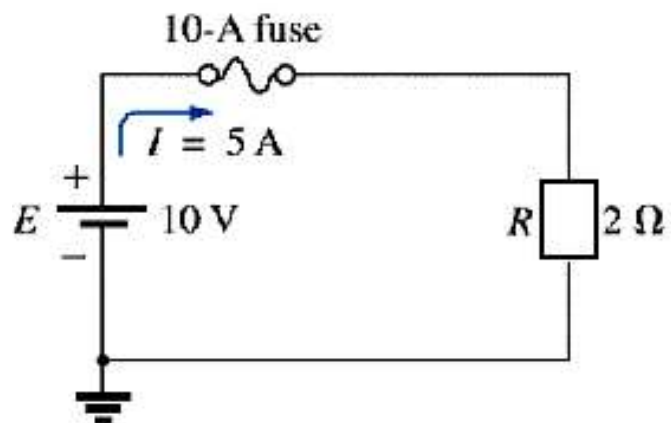

(a)

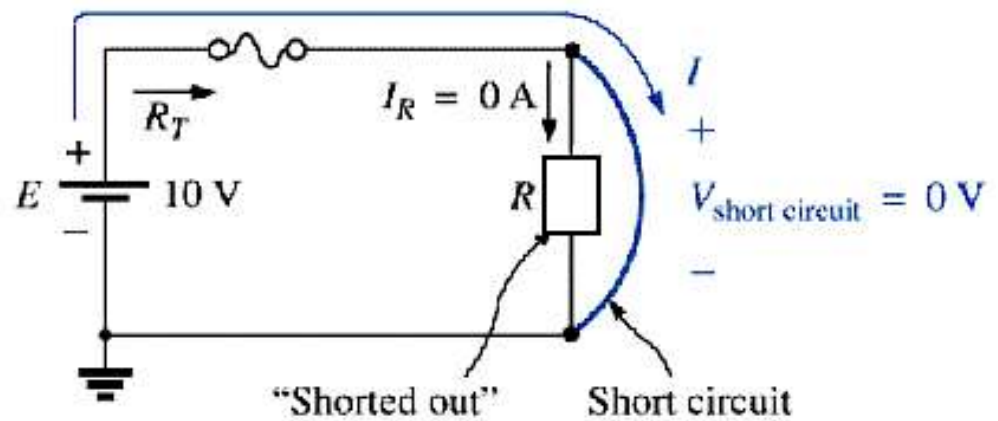

(b)

EXAMPLE

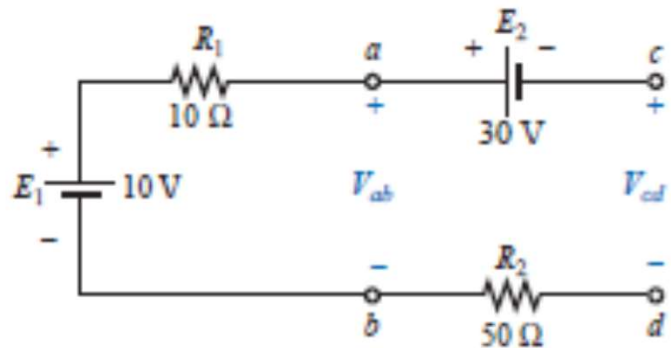


FIG. 6.46
Example 6.22.

EXAMPLE 6.22 Determine the voltages V_{ab} and V_{cd} for the network of Fig. 6.46.


Solution: The current through the system is zero amperes due to the open circuit, resulting in a 0-V drop across each resistor. Both resistors can therefore be replaced by short circuits, as shown in Fig. 6.47. The voltage V_{ab} is then directly across the 10-V battery, and

$$V_{ab} = E_1 = 10 \text{ V}$$

The voltage V_{cd} requires an application of Kirchhoff's voltage law:


$$+E_1 - E_2 - V_{cd} = 0$$

INTERNAL RESISTANCE OF A VOLTAGE SOURCE

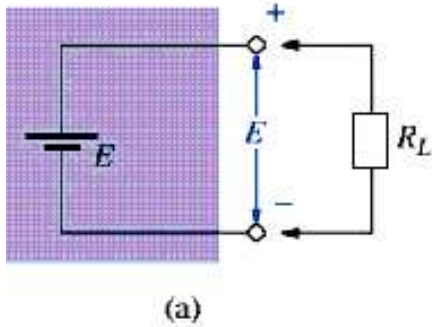


Ideal voltage source – no internal resistance

R_{int} = internal resistance of source

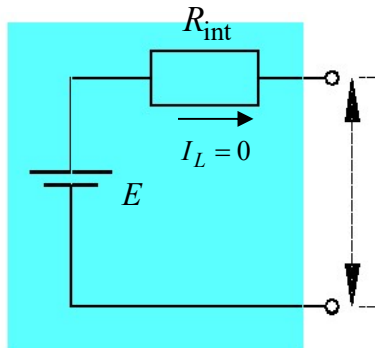

No Load Voltage

$$V_{NL} = E$$

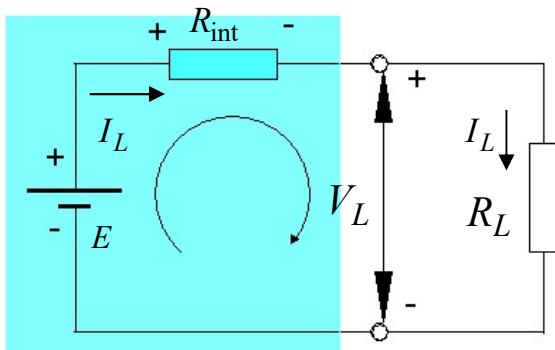


Load Voltage

$$V_L = \frac{R_L}{R_L + R_{\text{int}}} \cdot E$$

EXAMPLE

Find V_L and power loss in R_{int}

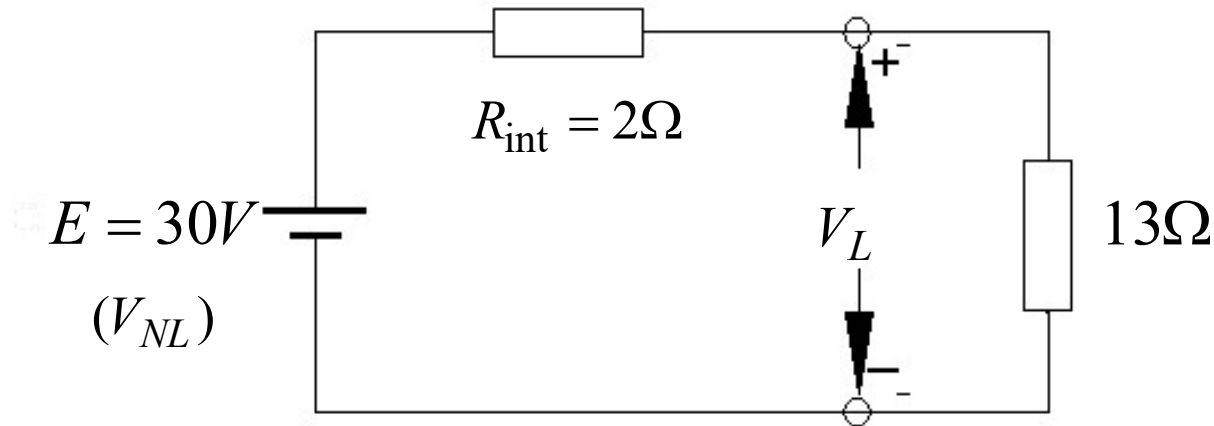

$$I_L = \frac{30V}{2\Omega + 13\Omega} = \frac{30V}{15\Omega} = 2A$$

$$V_L = V_{NL} - I_L \times R_{int} = 30V - (2A)(2\Omega) = 26V$$

$$P_{lost} = I_L^2 R_{int} = (2A)^2 (2\Omega) = (4)(2) = 8W$$

VOLTAGE REGULATION.

