


EEE 141 ELECTRICAL CIRCUITS

Dr. Shaikh Asif Mahmood
Associate professor, BUET

Adjunct Faculty, ECE, NSU





INDUCTORS

- Faraday's law
- Inductors
- R-L Transients
- Series and parallel inductors

FARADAY'S LAW

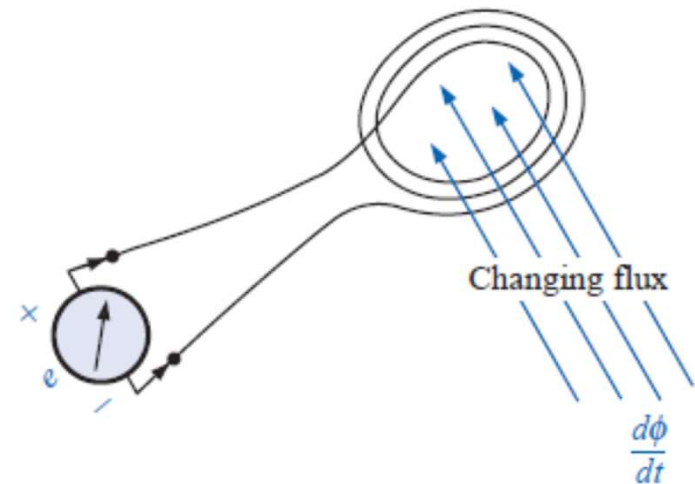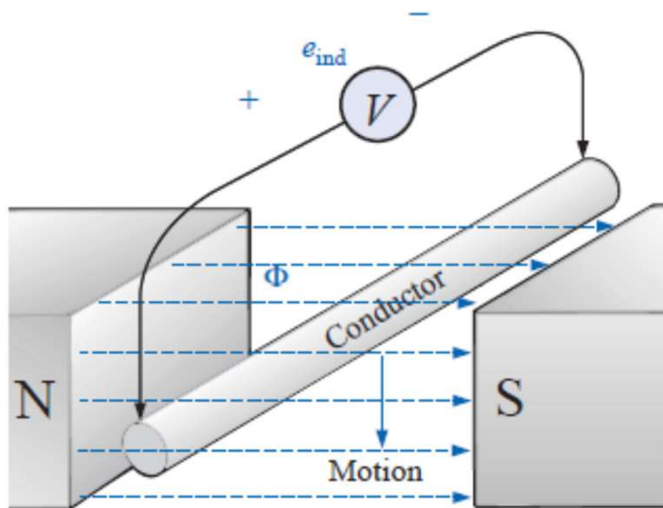- If a conductor is moved through a magnetic field so that it cuts magnetic lines of flux, a voltage will be induced across the conductor.
- If the conductor is held fixed and the magnetic field is moved so that its flux lines cut the conductor, the same effect will be produced.




FARADAY'S LAW

- If a coil of N turns is placed in the region of a changing flux, a voltage will be induced across the coil as determined by Faraday's law:

$$e = N \frac{d\phi}{dt} \quad (\text{volts, V}) \quad (12.1)$$

where N represents the number of turns of the coil and $d\phi/dt$ is the instantaneous change in flux (in webers) linking the coil. The term *linking* refers to the flux within the turns of wire. The term *changing* simply indicates that either the strength of the field linking the coil changes in magnitude or the coil is moved through the field in such a way that the number of flux lines through the coil changes with time.

LENZ'S LAW

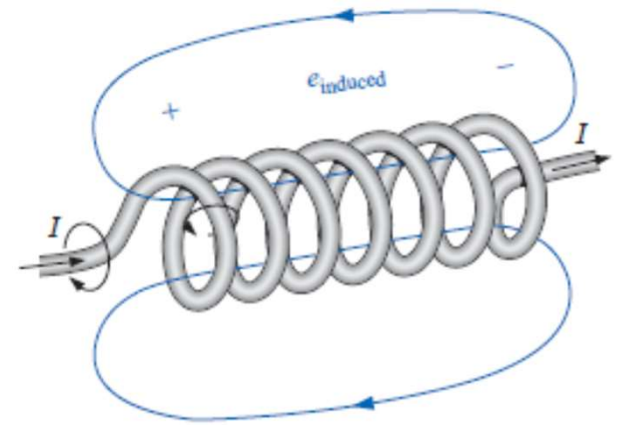


- The polarity of this induced voltage tends to establish a current in the coil that produces a flux that will oppose any change in the original flux.
- In other words, the induced effect (e_{ind}) is a result of the increasing current through the coil.
- However, the resulting induced voltage will tend to establish a current that will oppose the increasing change in current through the coil.
- An induced effect is always such as to oppose the cause that produced it.

INDUCTANCE



- The ability of a coil to oppose any change in current is a measure of the self-inductance L of the coil.
- Inductance is measured in henries (H).
- Inductors are coils of various dimensions designed to introduce specified amounts of inductance into a circuit.
- The inductance of a coil varies directly with the magnetic properties of the coil.
- Ferromagnetic materials, therefore, are frequently employed to increase the inductance by increasing the flux linking the coil.

INDUCTORS

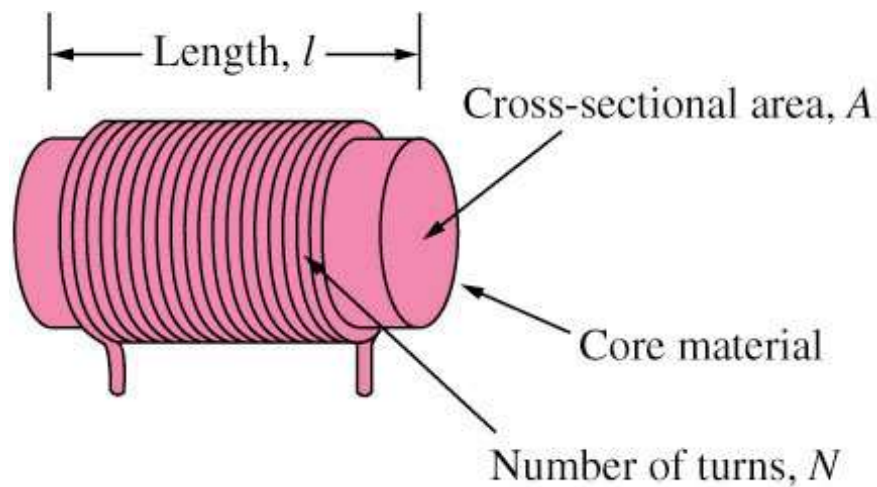An inductor is a passive element designed to store energy in its magnetic field.



$$L = \frac{N^2 \mu A}{l}$$

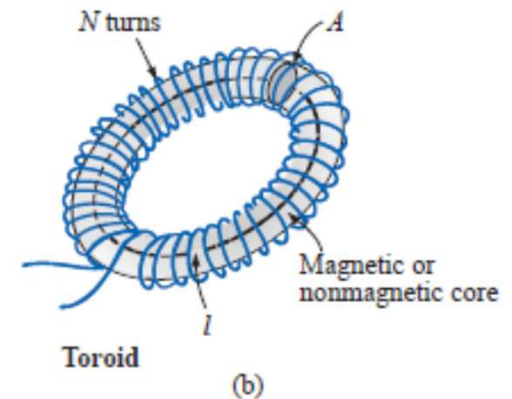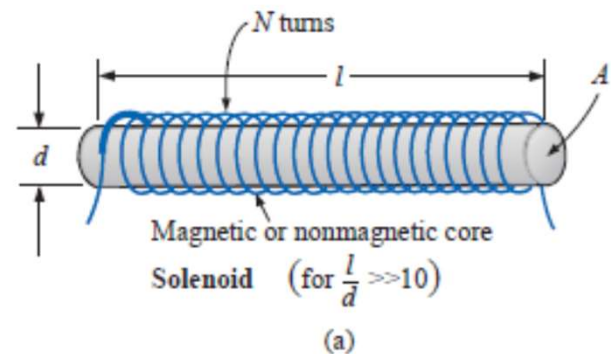

INDUCED VOLTAGE

The inductance of a coil is also a measure of the change in flux linking a coil due to a change in current through the coil.

$$L = N \frac{d\phi}{di} \quad (\text{H})$$

$$v = L \frac{di}{dt}$$

INDUCTORS


The current-voltage relationship of an inductor:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

- The energy stored by an inductor:


$$w = \frac{1}{2} L i^2$$

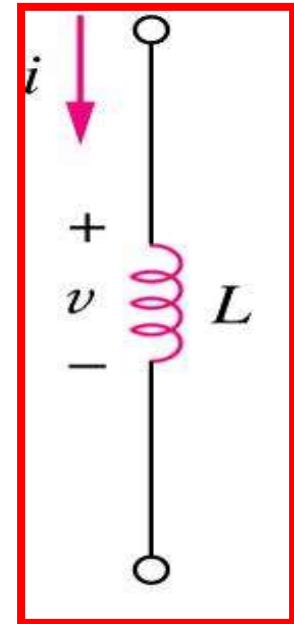- An inductor acts like a short circuit to dc ($di/dt = 0$) and its current cannot change abruptly.



INDUCTORS (EXAMPLE)

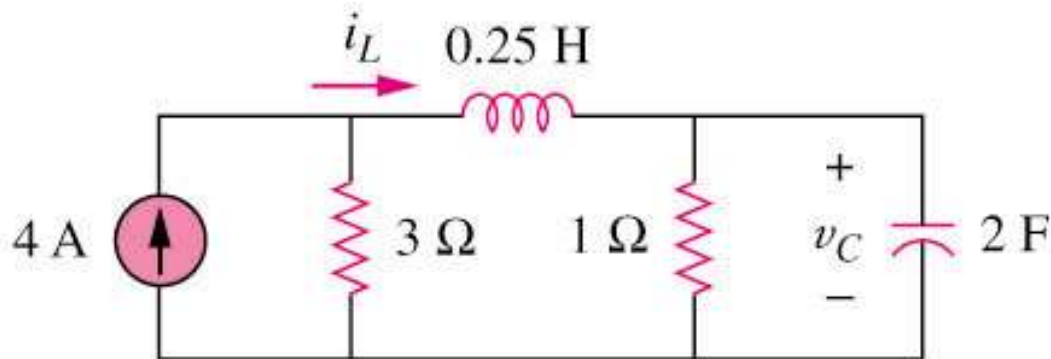Determine v_C , i_L , and the energy stored in the capacitor and inductor in the circuit of circuit shown below under dc conditions.



Answer:

$$i_L = 3\text{ A}$$

$$v_C = 3\text{ V}$$

$$w_L = 1.125\text{ J}$$

$$w_C = 9\text{ J}$$

R-L TRANSIENTS

- At the instant the switch is closed, the inductance of the coil will prevent an instantaneous change in current through the coil.
- The potential drop across the coil, v_L , will equal the impressed voltage E as determined by Kirchhoff's voltage law since $v_R = iR = 0$ V.

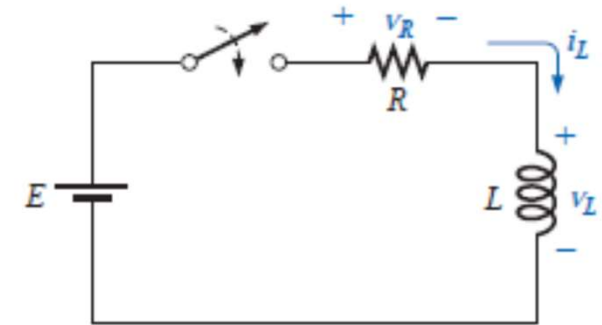


FIG. 12.14

Basic R-L transient network.

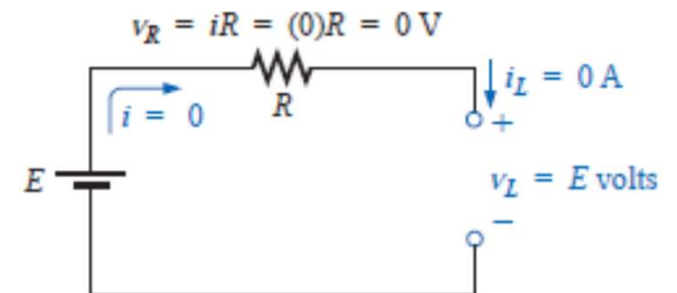



FIG. 12.15

Circuit of Fig. 12.14 the instant the switch is closed.

R-L TRANSIENTS


- The current will continue to increase until the voltage across the inductor drops to zero volts and the full impressed voltage appears across the resistor.
- An ideal inductor assumes a short-circuit equivalent in a dc network once steady-state conditions have been established.
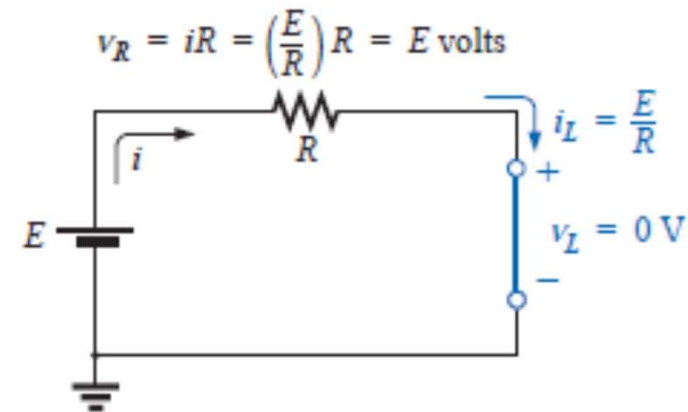
$$i_L = I_m(1 - e^{-t/\tau}) = \frac{E}{R}(1 - e^{-t/(L/R)})$$




SERIES AND PARALLEL INDUCTORS

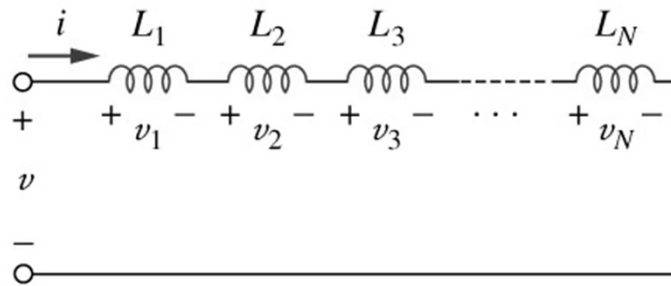The equivalent inductance of **series-connected** inductors is the sum of the individual inductances.



(a)

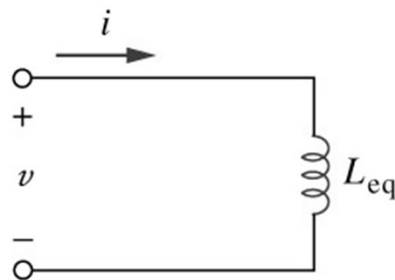


(b)

$$L_{eq} = L_1 + L_2 + \dots + L_N$$


SERIES AND PARALLEL INDUCTORS

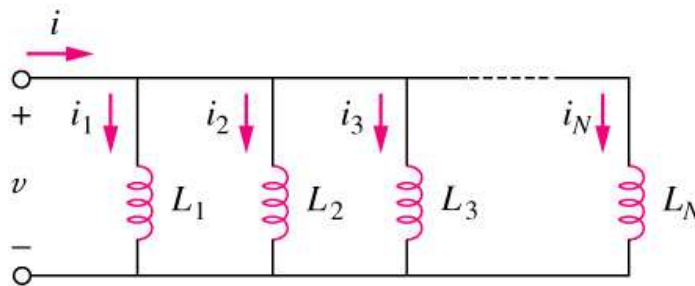The equivalent capacitance of **parallel** inductors is the reciprocal of the sum of the reciprocals of the individual inductances.



(a)

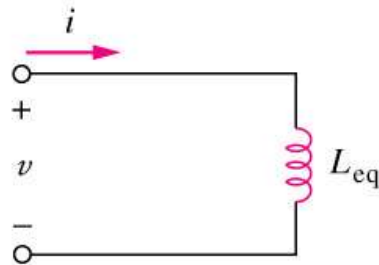
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$



(b)

SERIES AND PARALLEL INDUCTORS (EXAMPLE)

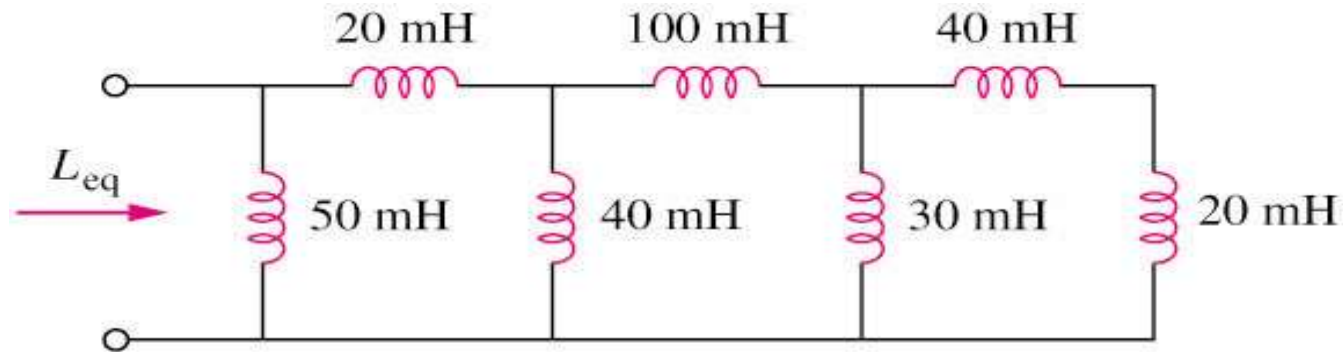


Calculate the equivalent inductance for the inductive ladder network in the circuit shown below:



Answer:

$$L_{eq} = \underline{25\text{mH}}$$

CURRENT AND VOLTAGE RELATIONSHIP FOR R, L, C

Circuit element	Units	Voltage	Current	Power
 Resistance	ohms (Ω)	$v = Ri$ (Ohm's law)	$i = \frac{v}{R}$	$p = vi = i^2 R$
 Inductance	henries (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt + k_1$	$p = vi = Li \frac{di}{dt}$
 Capacitance	farads (F)	$v = \frac{1}{C} \int i dt + k_2$	$i = C \frac{dv}{dt}$	$p = vi = Cv \frac{dv}{dt}$