


EEE 141 ELECTRICAL CIRCUITS

Dr. Shaikh Asif Mahmood
Associate professor, BUET

Adjunct Faculty, ECE, NSU




METHODS OF ANALYSIS

➤ Mesh Analysis

➤ Nodal Analysis

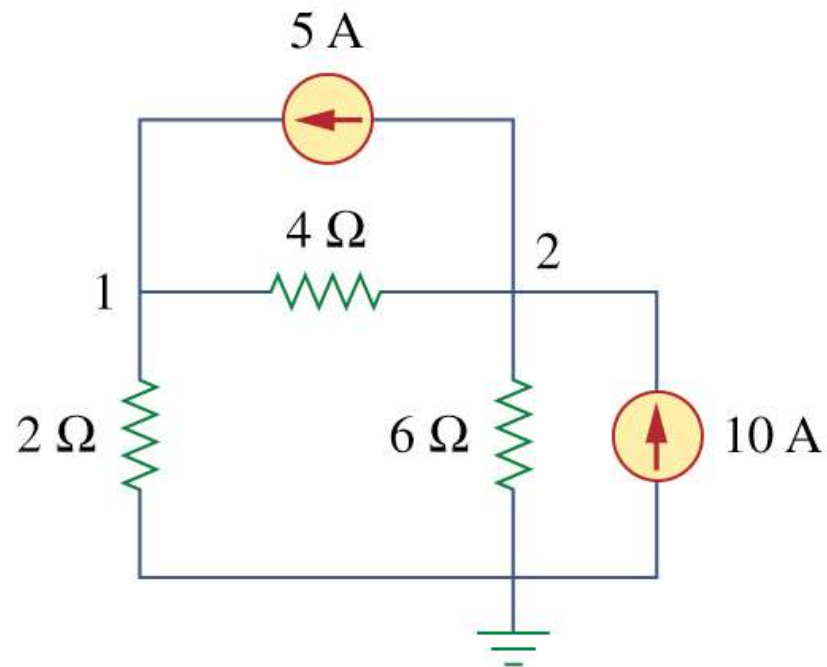EXAMPLE

Calculate the node voltage in the circuit shown in Fig(a)




(a)

EXAMPLE

At node 1

$$i_1 = i_2 + i_3$$
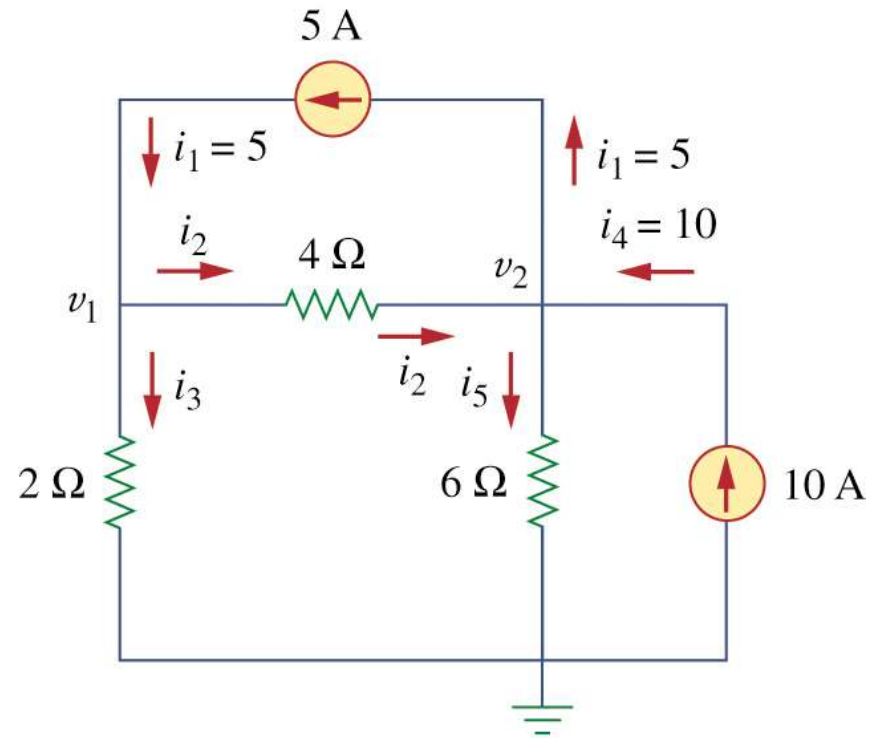
$$\Rightarrow 5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$




(b)

EXAMPLE

At node 2

$$i_2 + i_4 = i_1 + i_5$$
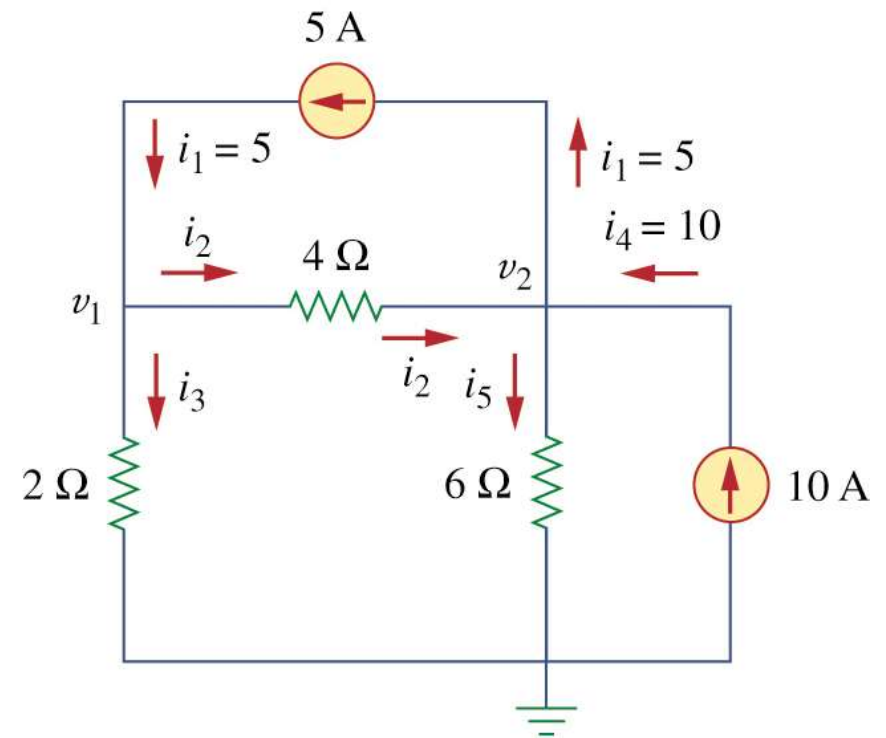
$$\Rightarrow 5 = \frac{v_2 - v_1}{4} + \frac{v_2 - 0}{6}$$



(b)

EXAMPLE

In matrix form:

$$\begin{bmatrix} \frac{1}{2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{6} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

EXAMPLE

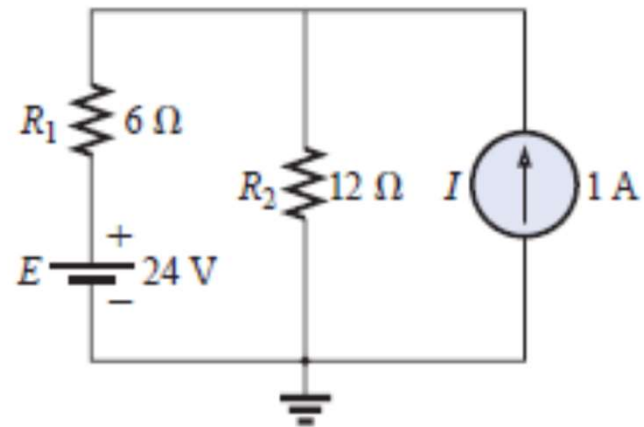


FIG. 8.40

Example 8.19.

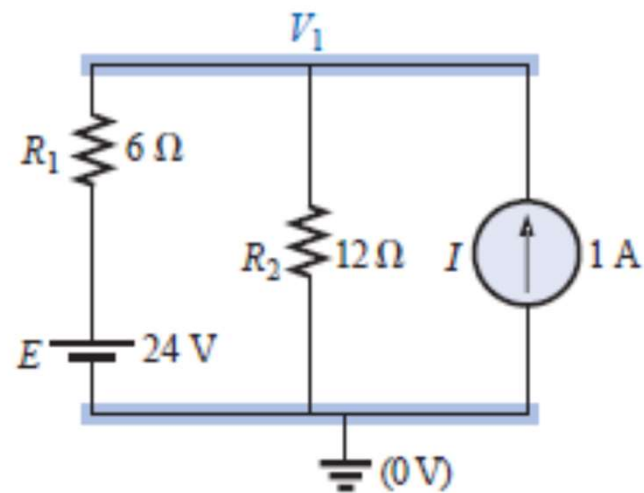


FIG. 8.41

Network of Fig. 8.40 with assigned nodes.

SOLUTION

$$I = I_1 + I_2$$

The current I_2 is related to the nodal voltage V_1 by Ohm's law:

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{V_1}{R_2}$$

The current I_1 is also determined by Ohm's law as follows:

$$I_1 = \frac{V_{R_1}}{R_1}$$

with

$$V_{R_1} = V_1 - E$$

Substituting into the Kirchhoff's current law equation:

$$I = \frac{V_1 - E}{R_1} + \frac{V_1}{R_2}$$

and rearranging, we have

$$I = \frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{E}{R_1}$$

or

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E}{R_1} + I$$

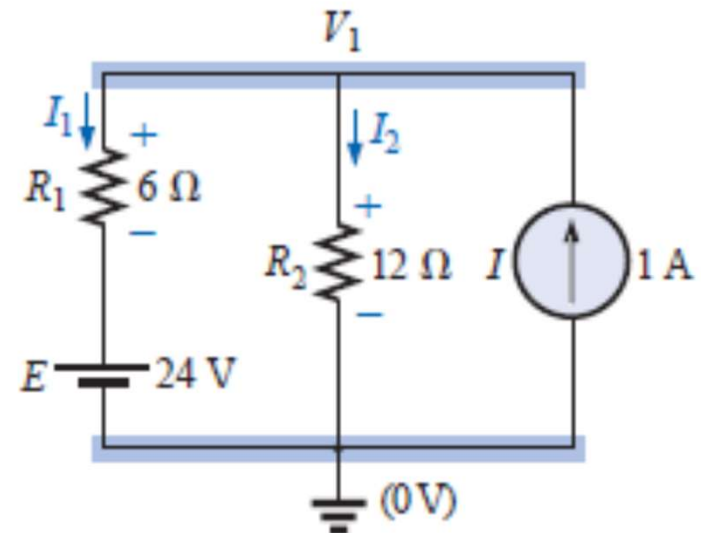


FIG. 8.42

Applying Kirchhoff's current law to the node V_1 .

SOLUTION

$$V_1 \left(\frac{1}{6 \, \Omega} + \frac{1}{12 \, \Omega} \right) = \frac{24 \, \text{V}}{6 \, \Omega} + 1 \, \text{A} = 4 \, \text{A} + 1 \, \text{A}$$



$$V_1 \left(\frac{1}{4 \, \Omega} \right) = 5 \, \text{A}$$

$$V_1 = 20 \, \text{V}$$

The currents I_1 and I_2 can then be determined using the preceding equations:

$$\begin{aligned} I_1 &= \frac{V_1 - E}{R_1} = \frac{20 \, \text{V} - 24 \, \text{V}}{6 \, \Omega} = \frac{-4 \, \text{V}}{6 \, \Omega} \\ &= -0.667 \, \text{A} \end{aligned}$$

EXAMPLE

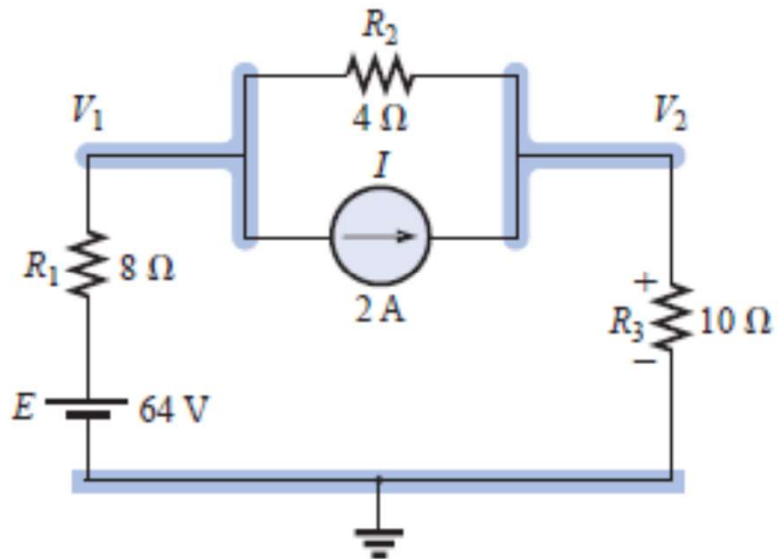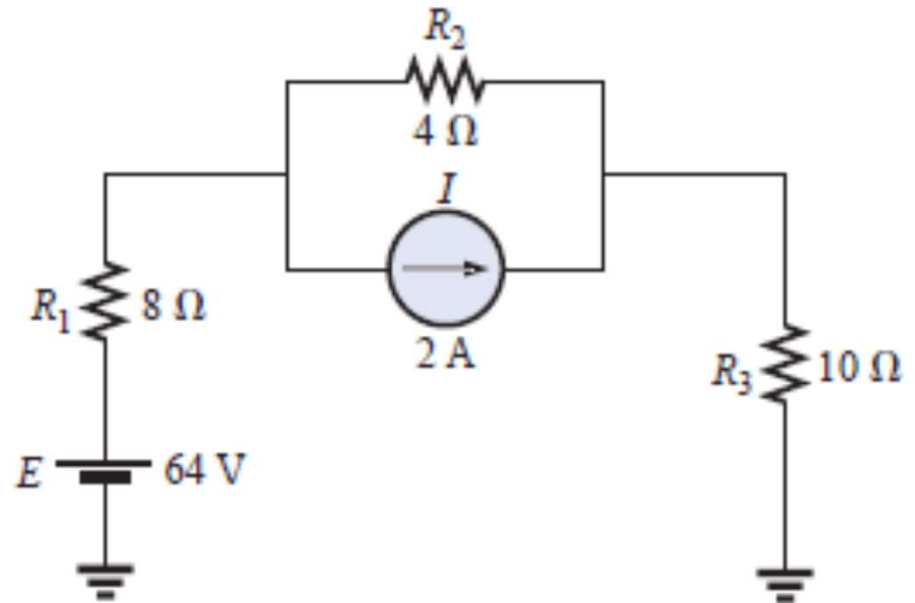

SOLUTION

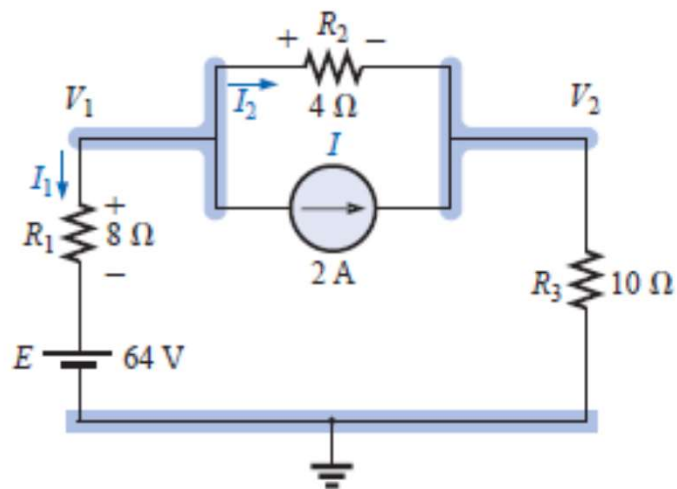


FIG. 8.45

Applying Kirchhoff's current law to node V_1 .

Step 3: For node V_1 the currents are defined as shown in Fig. 8.45, and Kirchhoff's current law is applied:

$$0 = I_1 + I_2 + I$$

$$I_1 = \frac{V_1 - E}{R_1}$$

with

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{V_1 - V_2}{R_2}$$

and

$$\frac{V_1 - E}{R_1} + \frac{V_1 - V_2}{R_2} + I = 0$$

so that

$$\frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + I = 0$$

or

$$\text{and} \quad V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{R_2} \right) = -I + \frac{E}{R_1}$$

Substituting values:

$$V_1 \left(\frac{1}{8 \Omega} + \frac{1}{4 \Omega} \right) - V_2 \left(\frac{1}{4 \Omega} \right) = -2 \text{ A} + \frac{64 \text{ V}}{8 \Omega} = 6 \text{ A}$$

SOLUTION

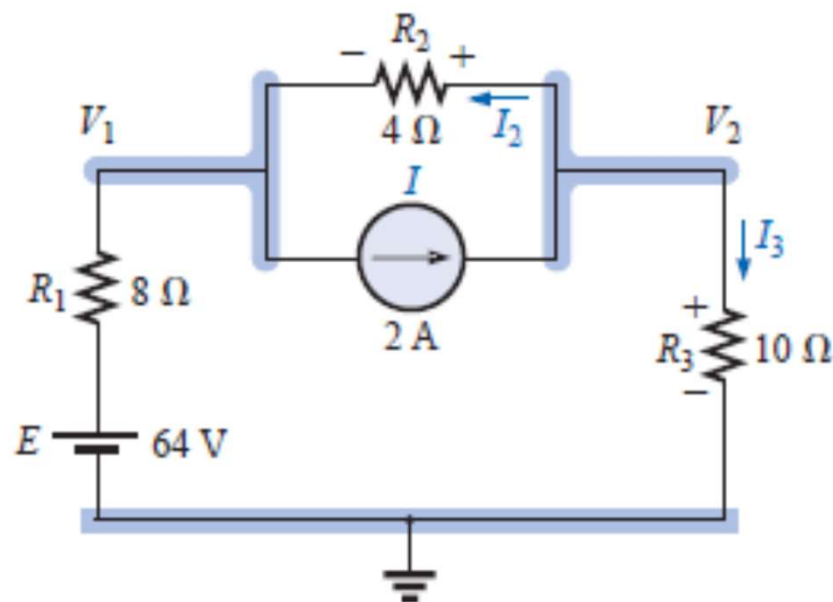


FIG. 8.46

Applying Kirchhoff's current law to node V_2

$$I = I_2 + I_3$$

$$I = \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3}$$

and

$$I = \frac{V_2}{R_2} - \frac{V_1}{R_2} + \frac{V_2}{R_3}$$

$$V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - V_1 \left(\frac{1}{R_2} \right) = I$$

Substituting values:

$$V_2 \left(\frac{1}{4 \Omega} + \frac{1}{10 \Omega} \right) - V_1 \left(\frac{1}{4 \Omega} \right) = 2 \text{ A}$$

Step 4: The result is two equations and two unknowns:

$$V_1 \left(\frac{1}{8 \Omega} + \frac{1}{4 \Omega} \right) - V_2 \left(\frac{1}{4 \Omega} \right) = 6 \text{ A}$$

$$-V_1 \left(\frac{1}{4 \Omega} \right) + V_2 \left(\frac{1}{4 \Omega} + \frac{1}{10 \Omega} \right) = 2 \text{ A}$$

which become

$$\begin{aligned} 0.375V_1 - 0.25V_2 &= 6 \\ -0.25V_1 + 0.35V_2 &= 2 \end{aligned}$$

Using determinants,

$$V_1 = 37.818 \text{ V}$$

$$V_2 = 32.727 \text{ V}$$

SOLUTION

$$I_{R_1} = \frac{E - V_1}{R_1} = \frac{64 \text{ V} - 37.818 \text{ V}}{8 \Omega} = 3.273 \text{ A}$$

The positive value for V_2 results in a current I_{R_3} from node V_2 to ground equal to

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{V_2}{R_3} = \frac{32.727 \text{ V}}{10 \Omega} = 3.273 \text{ A}$$

Since V_1 is greater than V_2 , the current I_{R_2} flows from V_1 to V_2 and is equal to

$$I_{R_2} = \frac{V_1 - V_2}{R_2} = \frac{37.818 \text{ V} - 32.727 \text{ V}}{4 \Omega} = 1.273 \text{ A}$$

EXAMPLE

EXAMPLE 8.21 Determine the nodal voltages for the network of Fig. 8.48.


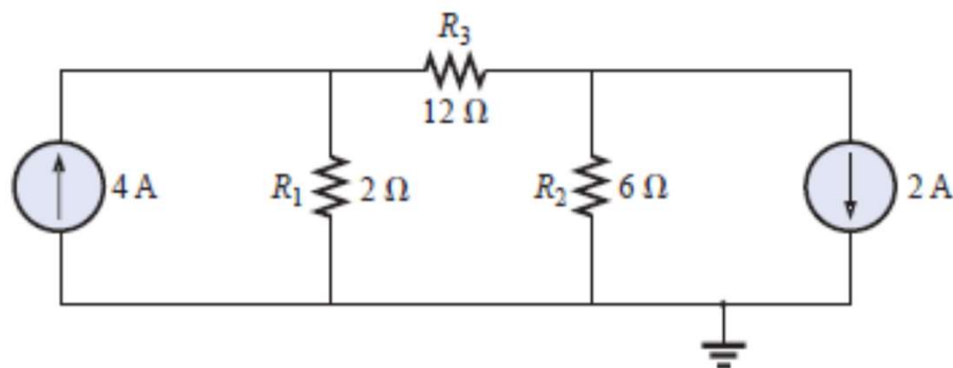



FIG. 8.48
Example 8.21.

Solution:

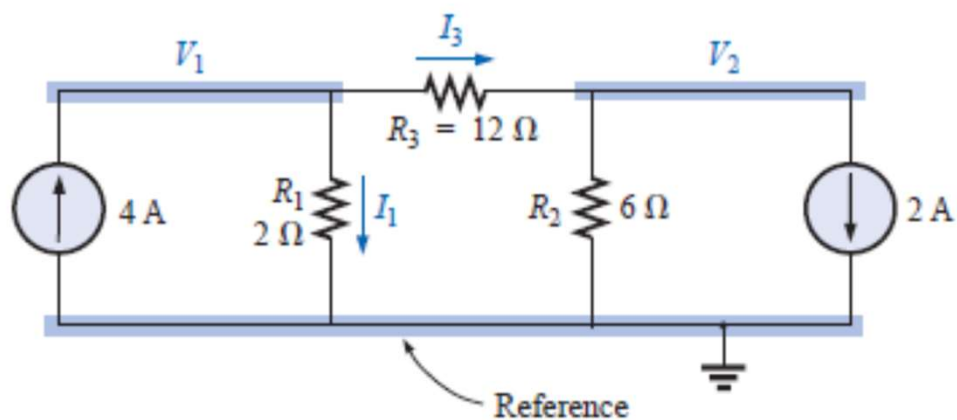Steps 1 and 2: As indicated in Fig. 8.49.



SOLUTION

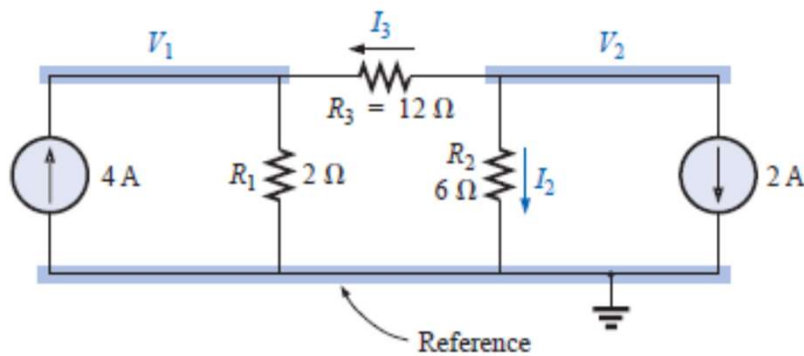

$$\left. \begin{aligned} V_1 \left(\frac{1}{2 \Omega} + \frac{1}{12 \Omega} \right) - V_2 \left(\frac{1}{12 \Omega} \right) &= +4 \text{ A} \\ V_2 \left(\frac{1}{12 \Omega} + \frac{1}{6 \Omega} \right) - V_1 \left(\frac{1}{12 \Omega} \right) &= -2 \text{ A} \end{aligned} \right\}$$

$$\left. \begin{aligned} \frac{7}{12} V_1 - \frac{1}{12} V_2 &= +4 \\ -\frac{1}{12} V_1 + \frac{3}{12} V_2 &= -2 \end{aligned} \right\} \begin{aligned} 7V_1 - V_2 &= 48 \\ -1V_1 + 3V_2 &= -24 \end{aligned}$$

$$V_1 = \frac{\begin{vmatrix} 48 & -1 \\ -24 & 3 \end{vmatrix}}{\begin{vmatrix} 7 & -1 \\ -1 & 3 \end{vmatrix}} = \frac{120}{20} = +6 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 7 & 48 \\ -1 & -24 \end{vmatrix}}{20} = \frac{-120}{20} = -6 \text{ V}$$


NODAL ANALYSIS WITH VOLTAGE SOURCES

Case 1: The voltage source is connected **between a nonreference node and the reference node**: The nonreference node voltage is equal to the magnitude of voltage source and the number of unknown nonreference nodes is reduced by one.

Case 2: The voltage source is connected **between two nonreferenced nodes**: a generalized node (**supernode**) is formed.

EXAMPLE

A circuit with a supernode.

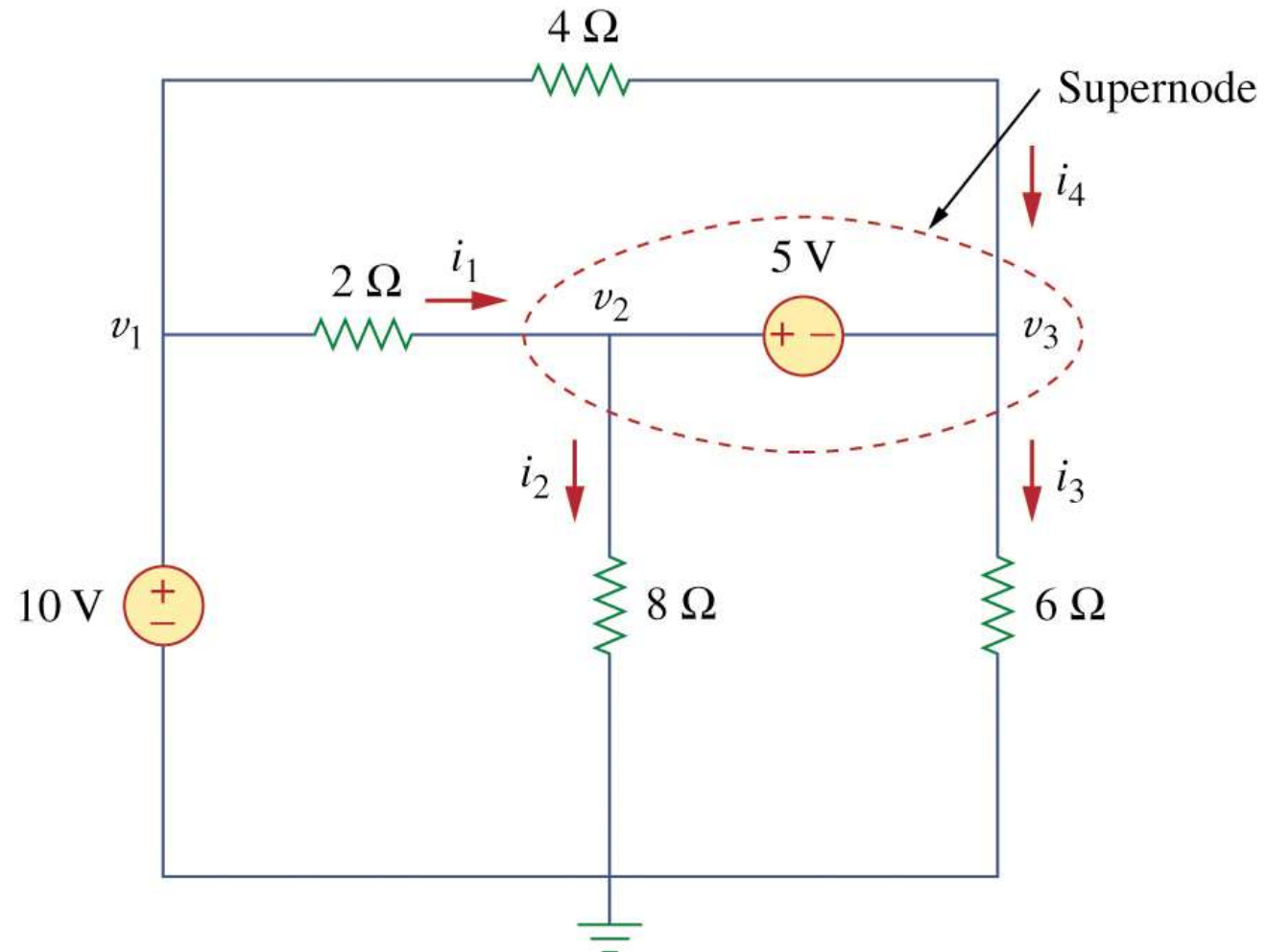


SUPERNODE

- A **supernode** is formed by **enclosing** a (dependent or independent) voltage source connected between two nonreference nodes and **any elements connected in parallel with it**.
- The required **two equations** for regulating the two nonreference node voltages are obtained by the KCL of the supernode and the **relationship of node voltages due to the voltage source**.

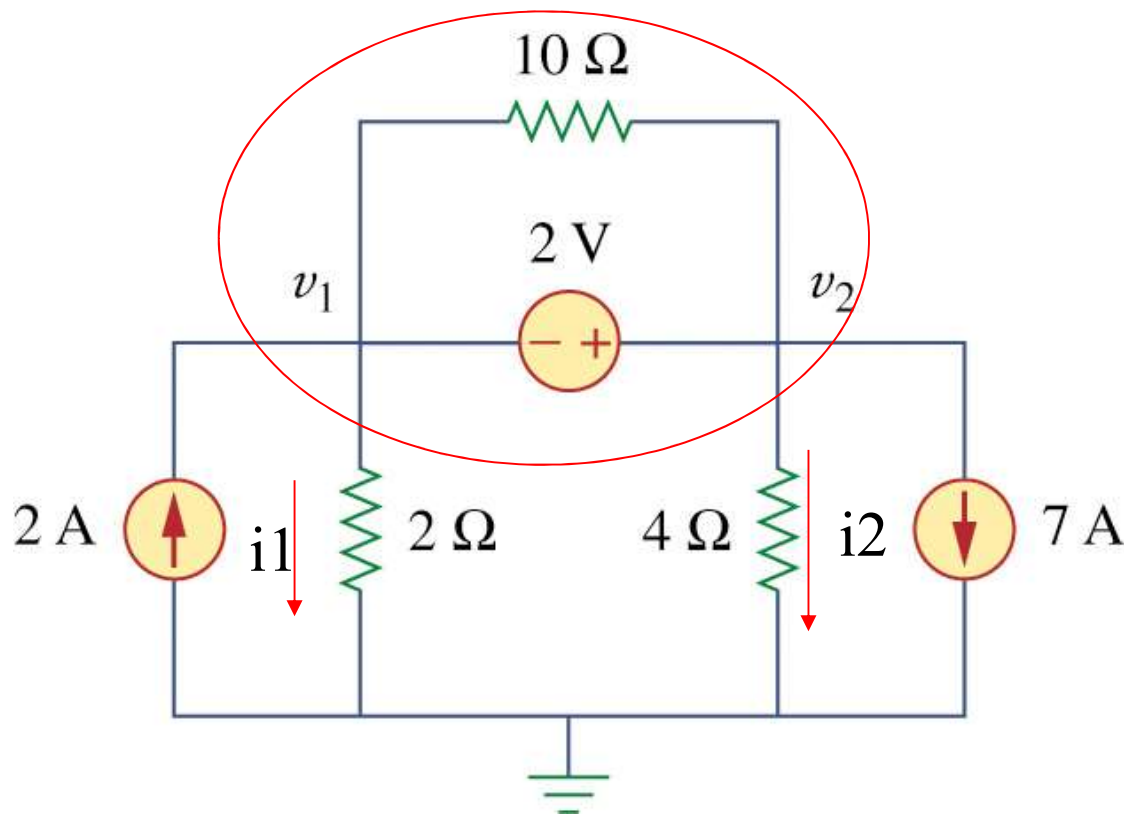EXAMPLE

For the circuit shown in Fig., find the node voltages.



$$2 - 7 - i1 - i2 = 0$$

$$2 - 7 - \frac{v_1}{2} - \frac{v_2}{4} = 0$$

$$v_1 - v_2 = -2$$

EXAMPLE

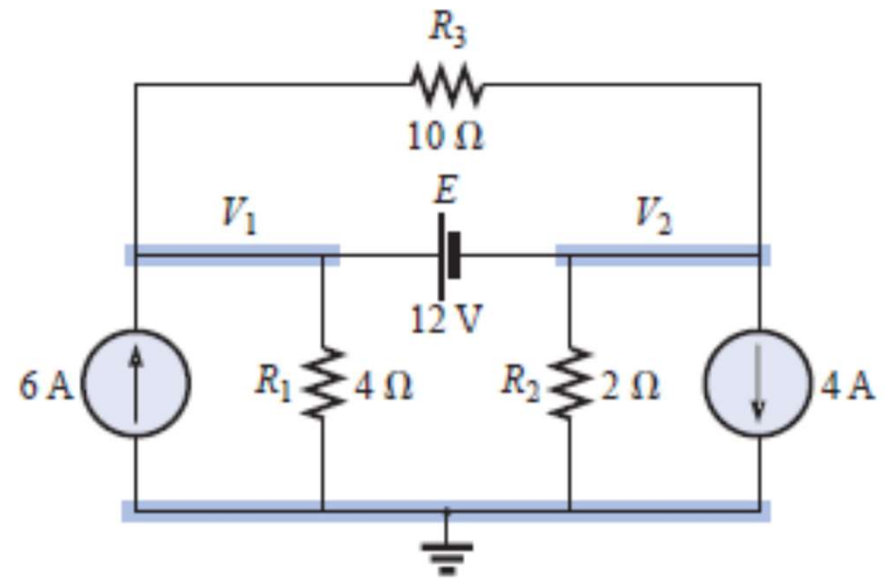


FIG. 8.51
Example 8.22.

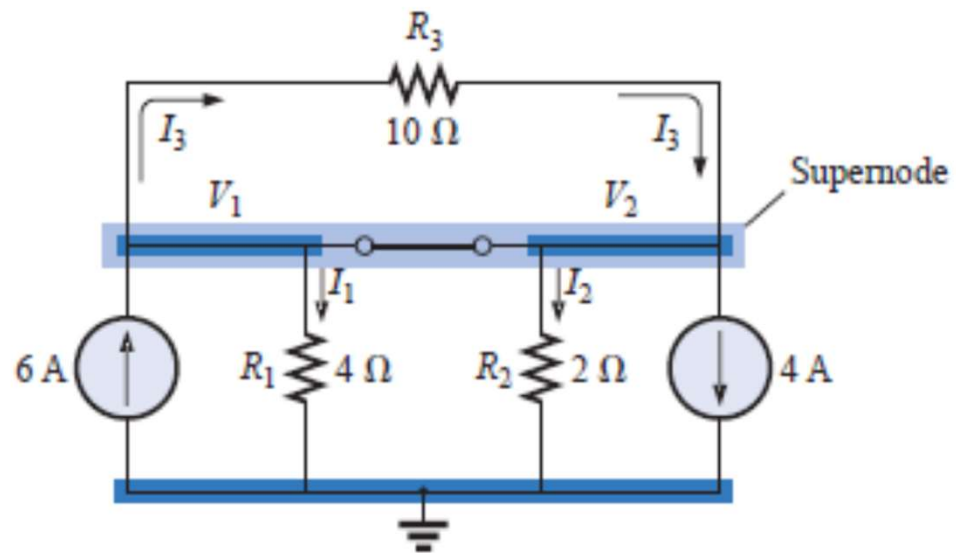


FIG. 8.52

Defining the supernode for the network of Fig. 8.51.

SOLUTION

and $V_1 = V_2 + 12 \text{ V} = -1.333 \text{ V} + 12 \text{ V} = +10.667 \text{ V}$

The current of the network can then be determined as follows:

$$I_1 \downarrow = \frac{V_1}{R_1} = \frac{10.667 \text{ V}}{4 \Omega} = 2.667 \text{ A}$$

$$I_2 \uparrow = \frac{V_2}{R_2} = \frac{1.333 \text{ V}}{2 \Omega} = 0.667 \text{ A}$$

$$I_3 \rightarrow = \frac{V_1 - V_2}{10 \Omega} = \frac{10.667 \text{ V} - (-1.333 \text{ V})}{10 \Omega} = \frac{12 \text{ V}}{10 \Omega} = 1.2 \text{ A}$$

$$6 \text{ A} + I_3 = I_1 + I_2 + 4 \text{ A} + I_3$$

$$I_1 + I_2 = 6 \text{ A} - 4 \text{ A} = 2 \text{ A}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = 2 \text{ A}$$

$$\frac{V_1}{4 \Omega} + \frac{V_2}{2 \Omega} = 2 \text{ A}$$

and nodal voltages to the independent

$$V_1 - V_2 = E = 12 \text{ V}$$

two equations and two unknowns:

$$\begin{array}{r} 0.25V_1 + 0.5V_2 = 2 \\ \underline{V_1 - 1V_2 = 12} \end{array}$$

$$V_1 = V_2 + 12$$

$$0.25(V_2 + 12) + 0.5V_2 = 2$$

$$0.75V_2 = 2 - 3 = -1$$

$$V_2 = \frac{-1}{0.75} = -1.333 \text{ V}$$

EXAMPLE


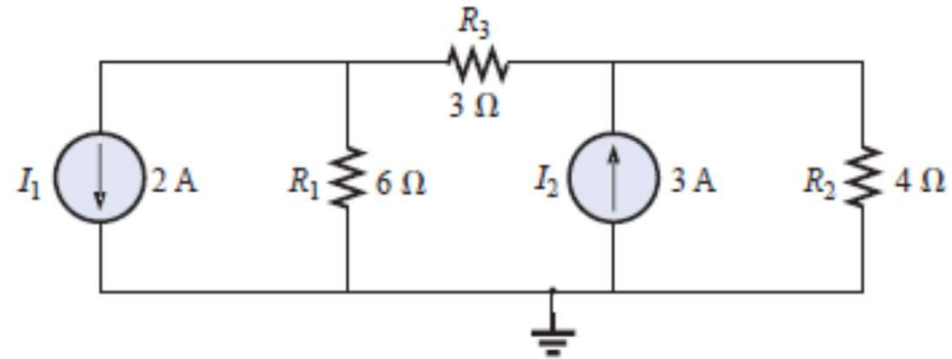


FIG. 8.53
Example 8.23.

Solution:

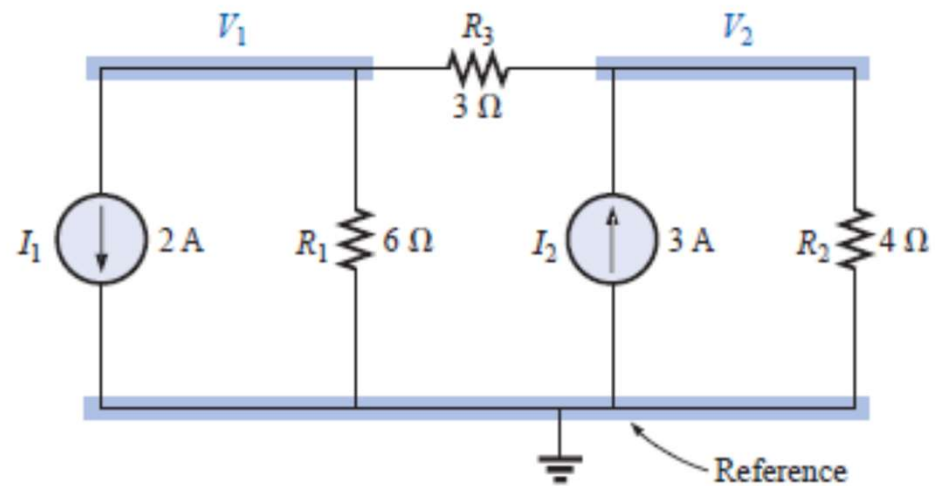Step 1: The figure is redrawn with assigned subscripted voltages in Fig. 8.54.



SOLUTION

$$V_1: \underbrace{\left(\frac{1}{6\ \Omega} + \frac{1}{3\ \Omega} \right)}_{\text{Sum of conductances connected to node 1}} V_1 - \underbrace{\left(\frac{1}{3\ \Omega} \right)}_{\text{Mutual conductance}} V_2 = \overset{\substack{\text{Drawing current} \\ \text{from node 1}}}{\downarrow} -2\ \text{A}$$

$$V_2: \underbrace{\left(\frac{1}{4\ \Omega} + \frac{1}{3\ \Omega} \right)}_{\text{Sum of conductances connected to node 2}} V_2 - \underbrace{\left(\frac{1}{3\ \Omega} \right)}_{\text{Mutual conductance}} V_1 = \overset{\substack{\text{Supplying current} \\ \text{to node 2}}}{\downarrow} +3\ \text{A}$$

$$\frac{1}{2}V_1 - \frac{1}{3}V_2 = -2$$

$$\underline{-\frac{1}{3}V_1 + \frac{7}{12}V_2 = 3}$$

EXAMPLE

EXAMPLE 8.24 Find the voltage across the $3\text{-}\Omega$ resistor of Fig. 8.55 by nodal analysis.

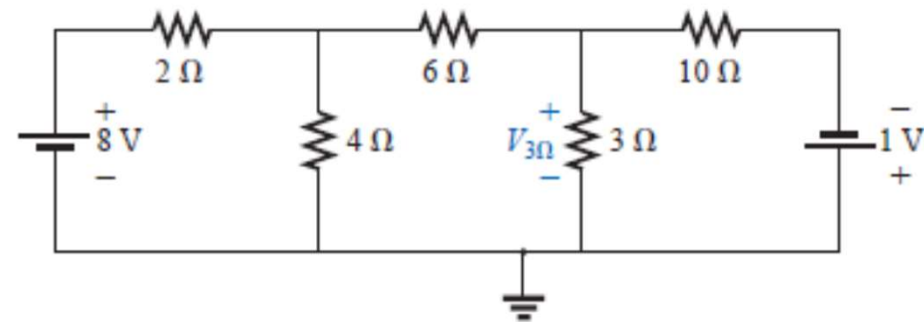


FIG. 8.55
Example 8.24.

Solution: Converting sources and choosing nodes (Fig. 8.56), we have

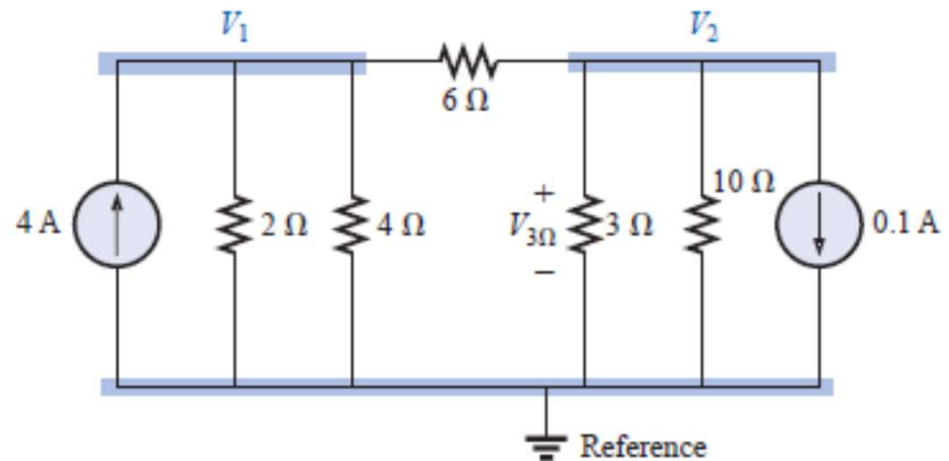


FIG. 8.56
Defining the nodes for the network of Fig. 8.55.

SOLUTION

$$\left. \begin{aligned} \left(\frac{1}{2\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{6\ \Omega} \right) V_1 - \left(\frac{1}{6\ \Omega} \right) V_2 &= +4\ \text{A} \\ \left(\frac{1}{10\ \Omega} + \frac{1}{3\ \Omega} + \frac{1}{6\ \Omega} \right) V_2 - \left(\frac{1}{6\ \Omega} \right) V_1 &= -0.1\ \text{A} \end{aligned} \right\}$$

$$\frac{11}{12} V_1 - \frac{1}{6} V_2 = 4$$

$$-\frac{1}{6} V_1 + \frac{3}{5} V_2 = -0.1$$

resulting in

$$11V_1 - 2V_2 = +48$$

$$-5V_1 + 18V_2 = -3$$

and

$$V_2 = V_{3\Omega} = \frac{\begin{vmatrix} 11 & 48 \\ -5 & -3 \end{vmatrix}}{\begin{vmatrix} 11 & -2 \\ -5 & 18 \end{vmatrix}} = \frac{-33 + 240}{198 - 10} = \frac{207}{188} = \mathbf{1.101\ V}$$