


EEE 141 ELECTRICAL CIRCUITS

Dr. Shaikh Asif Mahmood
Associate professor, BUET

Adjunct Faculty, ECE, NSU



BASIC LAWS

Nodes, Branches, and Loops.

Kirchhoff's Laws.

Series Resistors and Voltage Division.

Parallel Resistors and Current Division.

NODES, BRANCHES AND LOOPS

A **branch** represents a single element such as a voltage source or a resistor.

A **node** is the point of connection between two or more branches.



A **loop** is any closed path in a circuit.

A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology:

$$b = l + n - 1$$

NODES, BRANCHES AND LOOPS

Exc

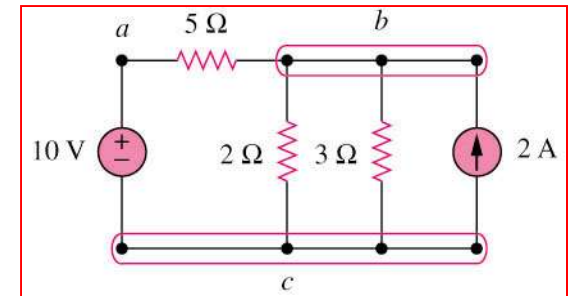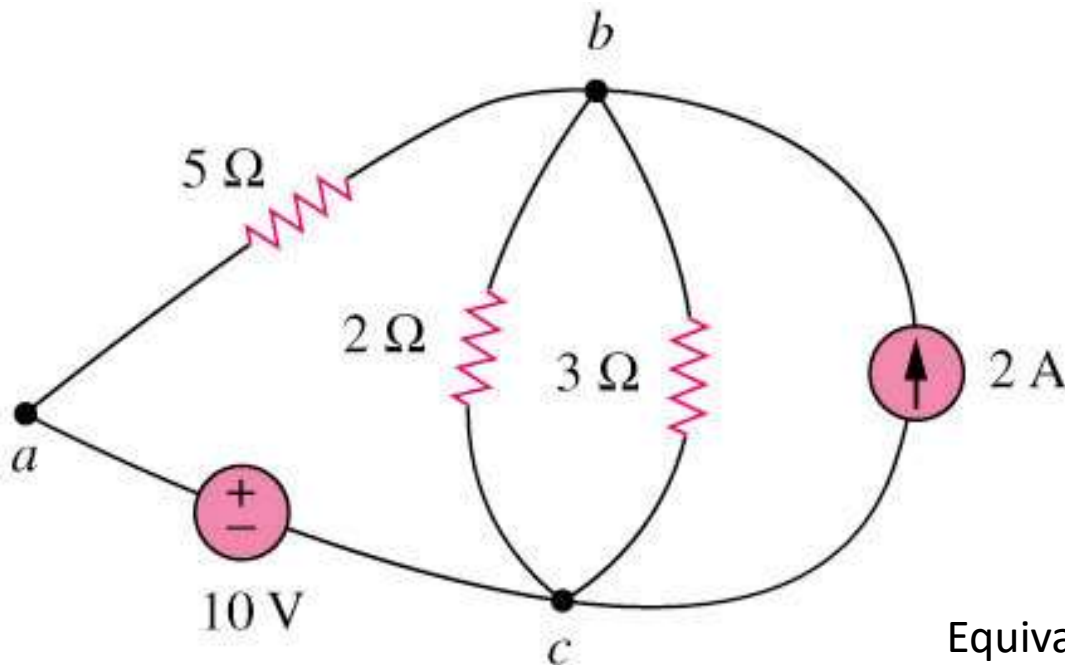


Original circuit

Equivalent circuit

How many branches, nodes and loops are there?


Series and Parallel Connections

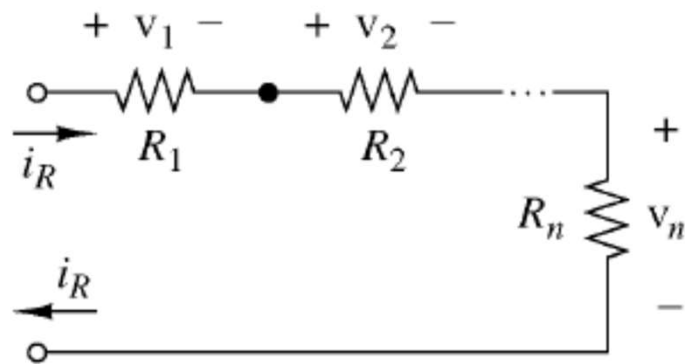- Two or more elements are connected “**in series**” when they belong to the same branch.(even if they are separated by other elements).
- In general, circuit elements are in series when they are sequentially connected end-to-end and only share binary nodes among them.
- Elements that are in series carry the same current.




Series and Parallel Circuits

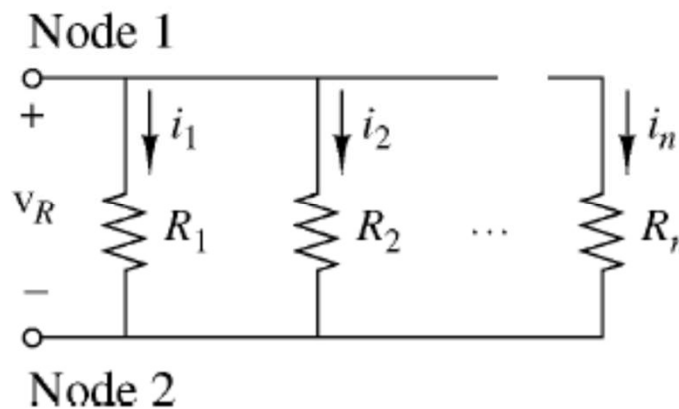- Two or more circuit elements are “**in parallel**” if they are connected between the same two “true nodes”.
- Consequently, parallel elements have the same voltage




KIRCHHOFF'S LAWS

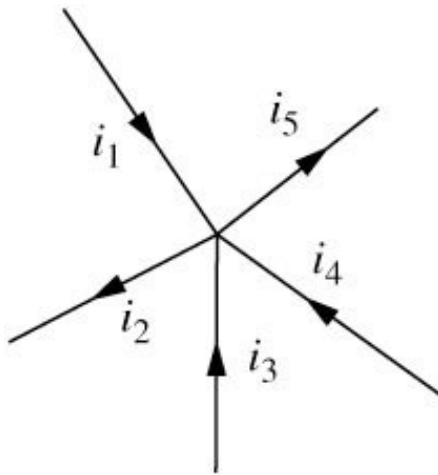Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.




Mathematically,

$$\sum_{n=1}^N i_n = 0$$

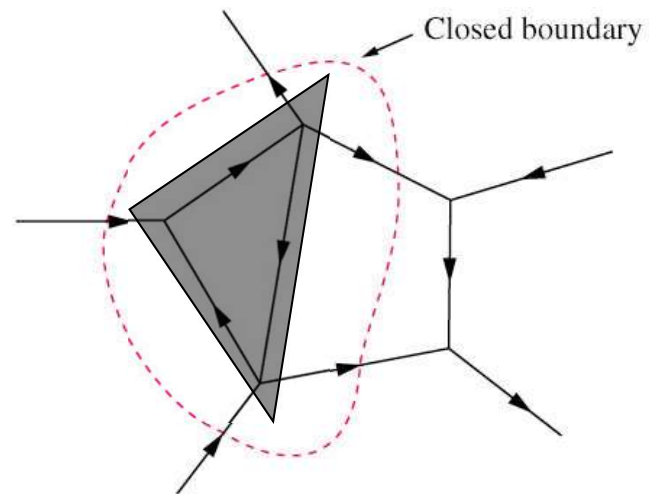

KIRCHHOFF'S LAWS

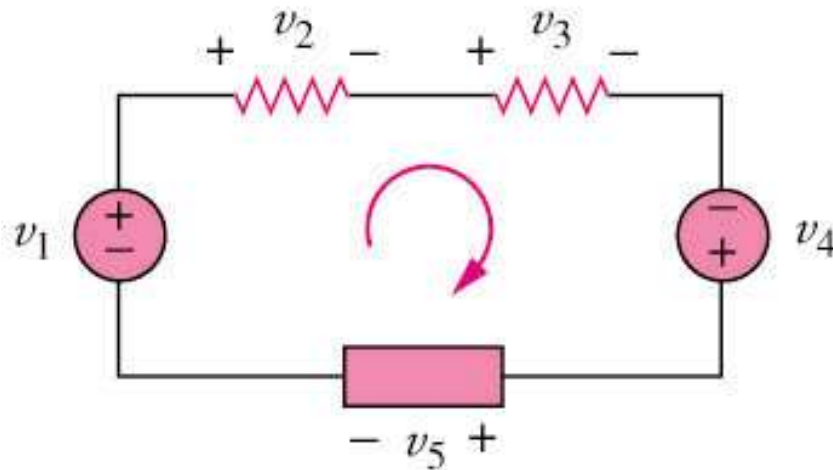Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.




Mathematically,


$$\sum_{m=1}^M v_n = 0$$

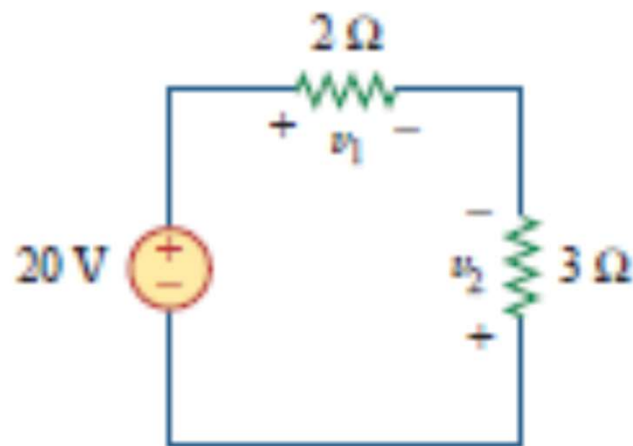EXAMPLE

For the circuit in Fig. 2.21(a), find voltages v_1 and v_2 .



(a)

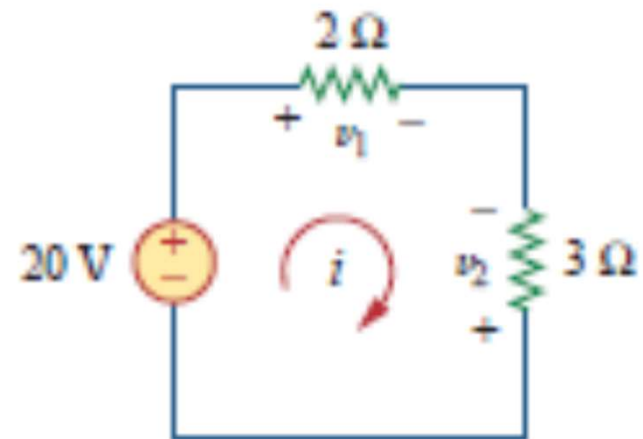

(b)

Figure 2.21
For Example 2.5.

EXAMPLE

Determine v_o and i in the circuit shown in Fig. 2.23(a).

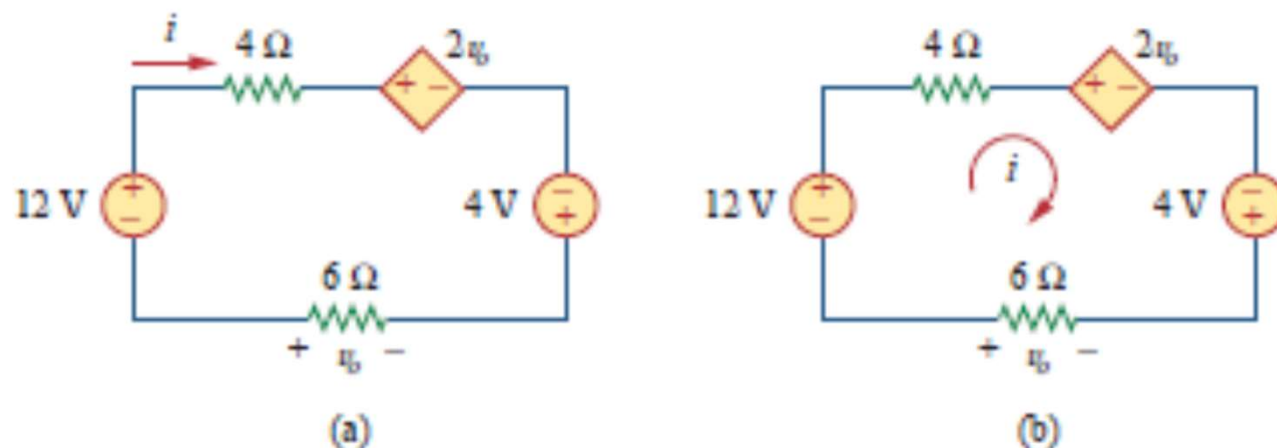


Figure 2.23
For Example 2.6.

Solution:

We apply KVL around the loop as shown in Fig. 2.23(b). The result is

$$-12 + 4i + 2v_o - 4 + 6i = 0 \quad (2.6.1)$$

Applying Ohm's law to the 6-Ω resistor gives

$$v_o = -6i \quad (2.6.2)$$

EXAMPLE

Example 2.7

Find current i_o and voltage v_o in the circuit shown in Fig. 2.25.

Solution:

Applying KCL to node a , we obtain

$$3 + 0.5i_o = i_o \quad \Rightarrow \quad i_o = 6 \text{ A}$$

For the $4\text{-}\Omega$ resistor, Ohm's law gives

$$v_o = 4i_o = 24 \text{ V}$$

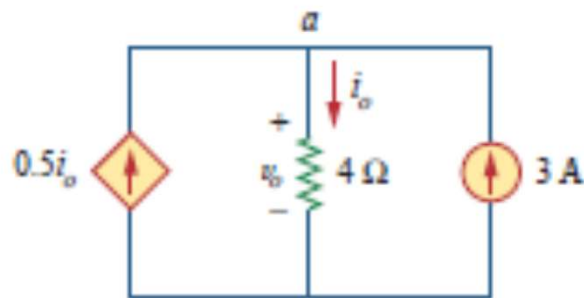


Figure 2.25
For Example 2.7.

EXAMPLE

Example 2.8

Find currents and voltages in the circuit shown in Fig. 2.27(a).

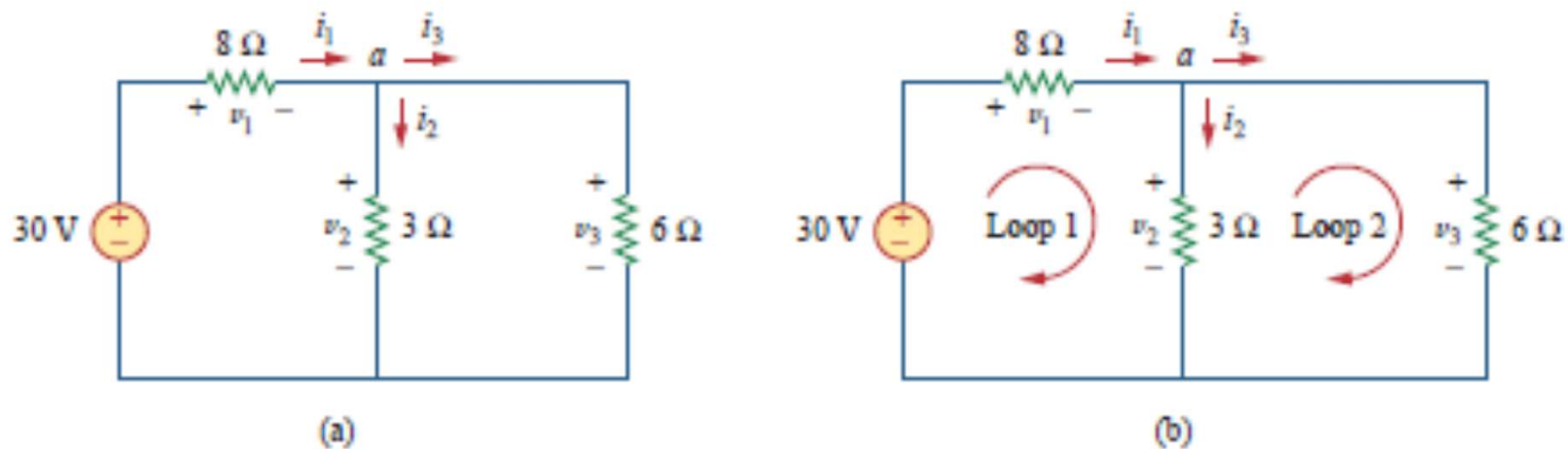


Figure 2.27
For Example 2.8.

Solution:

We apply Ohm's law and Kirchhoff's laws. By Ohm's law,

$$v_1 = 8i_1, \quad v_2 = 3i_2, \quad v_3 = 6i_3 \quad (2.8.1)$$

SERIES RESISTORS AND VOLTAGE DIVISION (1)

Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.

The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances.

$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

The voltage divider can be expressed as

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

EXAMPLE

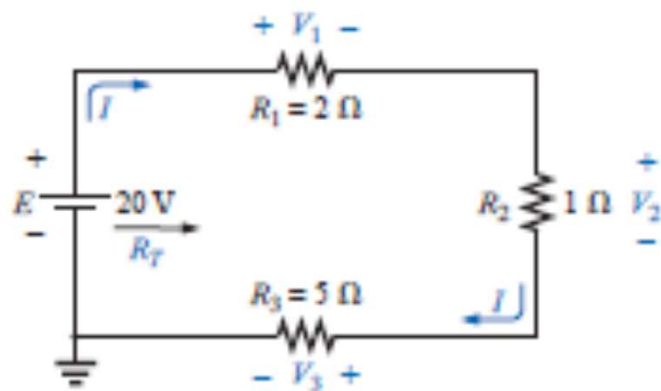


FIG. 5.7
Example 5.1.

EXAMPLE 5.1


- Find the total resistance for the series circuit of Fig. 5.7.
- Calculate the source current I_s .
- Determine the voltages V_1 , V_2 , and V_3 .
- Calculate the power dissipated by R_1 , R_2 , and R_3 .
- Determine the power delivered by the source, and compare it to the sum of the power levels of part (d).

Solutions:

a. $R_T = R_1 + R_2 + R_3 = 2\ \Omega + 1\ \Omega + 5\ \Omega = 8\ \Omega$

b. $I_s = \frac{E}{R_T} = \frac{20\ \text{V}}{8\ \Omega} = 2.5\ \text{A}$

EXAMPLE

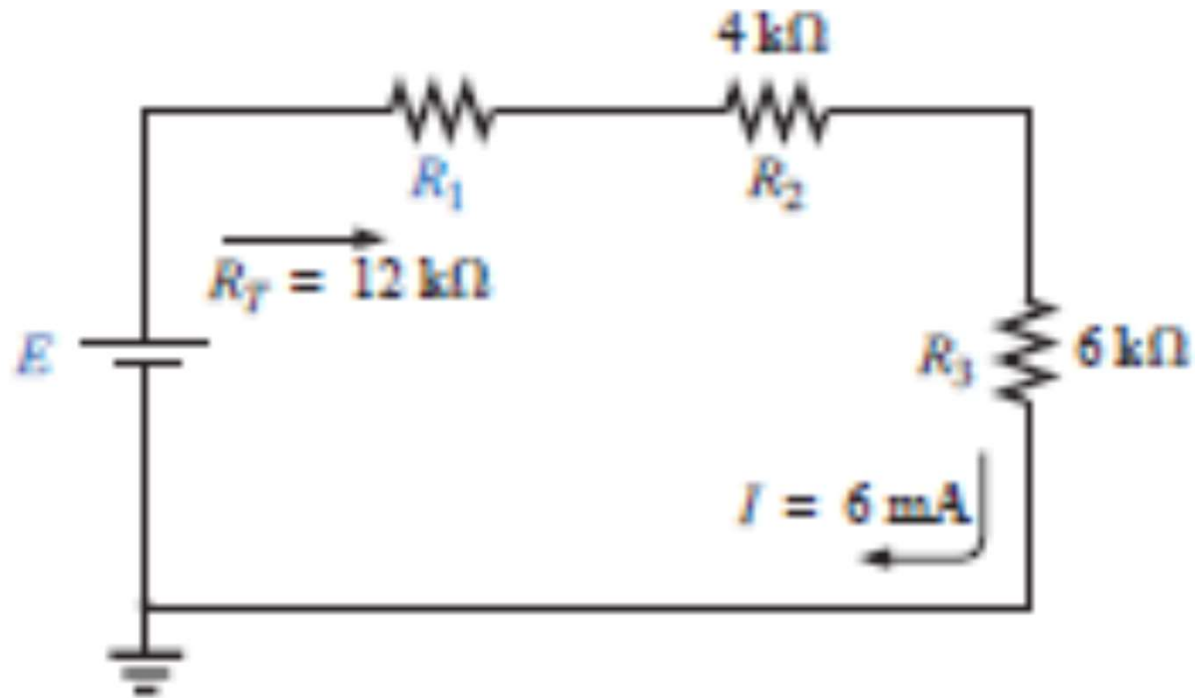

EXAMPLE


EXAMPLE 5.11 Using the voltage divider rule, determine the voltages V_1 and V_3 for the series circuit of Fig. 5.28.

Solution:

$$V_1 = \frac{R_1 E}{R_T} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega}$$
$$= \frac{(2 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega} = \frac{90 \text{ V}}{15} = 6 \text{ V}$$

$$V_3 = \frac{R_3 E}{R_T} = \frac{(8 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega} = \frac{(8 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega}$$
$$= \frac{360 \text{ V}}{15} = 24 \text{ V}$$

FIG. 5.27
Example 5.10.

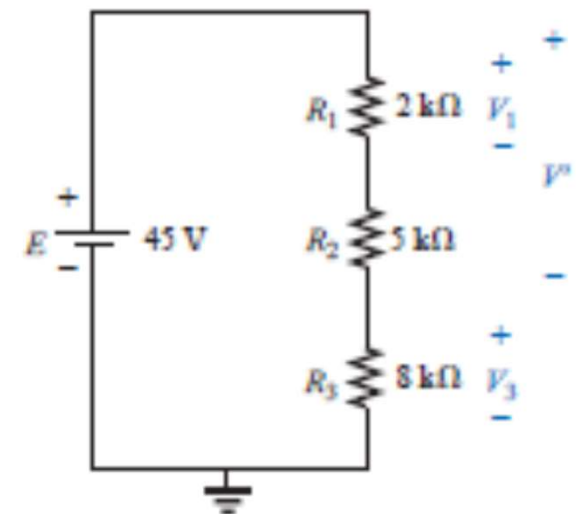

EXAMPLE

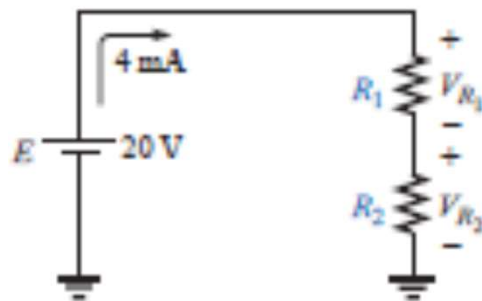


FIG. 5.30
Example 5.13.

EXAMPLE 5.13 Design the voltage divider of Fig. 5.30 such that $V_{R_1} = 4V_{R_2}$.

Solution: The total resistance is defined by

$$R_T = \frac{E}{I} = \frac{20\text{ V}}{4\text{ mA}} = 5\text{ k}\Omega$$

Since $V_{R_1} = 4V_{R_2}$

$$R_1 = 4R_2$$

Thus

$$R_T = R_1 + R_2 = 4R_2 + R_2 = 5R_2$$

and

$$5R_2 = 5\text{ k}\Omega$$

$$R_2 = 1\text{ k}\Omega$$

and

$$R_1 = 4R_2 = 4\text{ k}\Omega$$

INTERCHANGING SERIES ELEMENTS

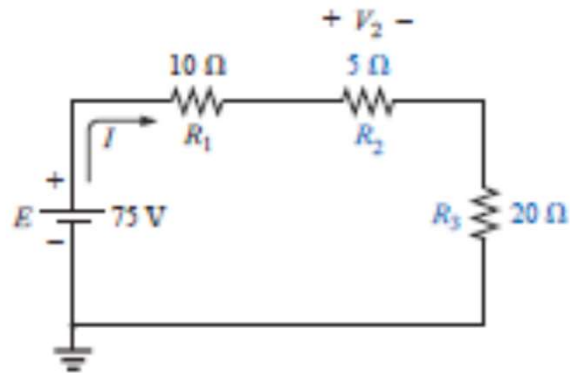


FIG. 5.19

Series dc circuit with elements to be interchanged.


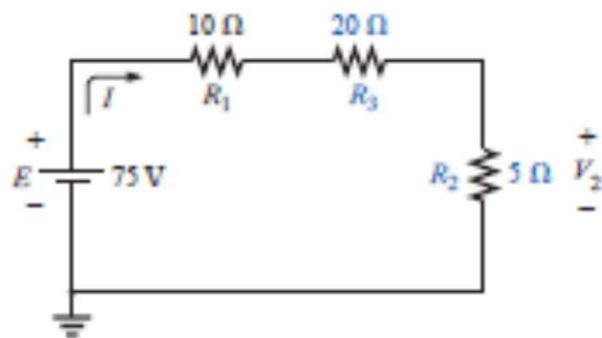


FIG. 5.20

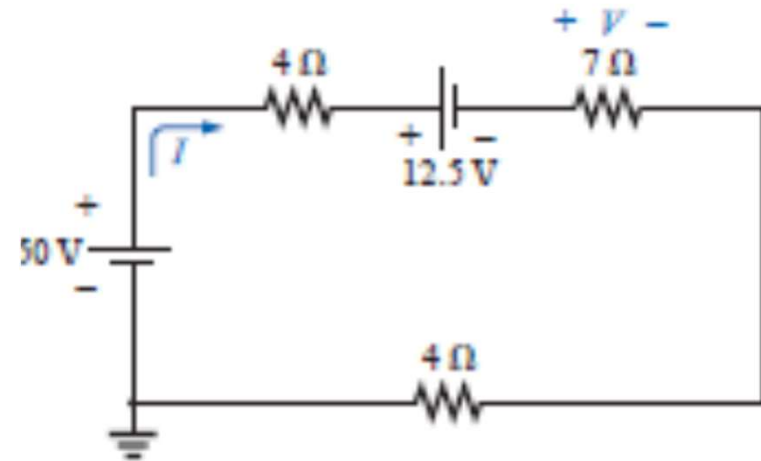Circuit of Fig. 5.19 with R_2 and R_3 interchanged.



EXAMPLE

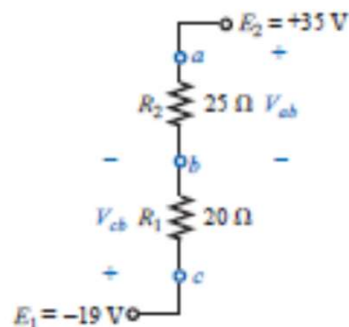


FIG. 5.45
Example 5.18.

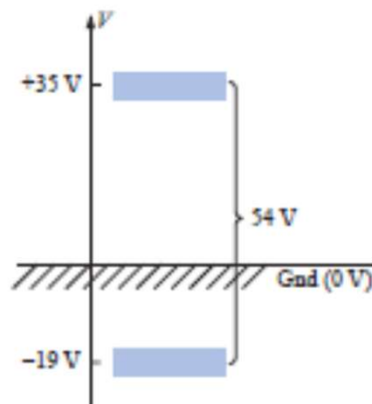


FIG. 5.46

EXAMPLE 5.18 Determine V_{ab} , V_{cb} , and V_c for the network of Fig. 5.45.

Solution: There are two ways to approach this problem. The first is to sketch the diagram of Fig. 5.46 and note that there is a 54-V drop across the series resistors R_1 and R_2 . The current can then be determined using Ohm's law and the voltage levels as follows:

$$I = \frac{54 \text{ V}}{45 \Omega} = 1.2 \text{ A}$$

$$V_{ab} = IR_2 = (1.2 \text{ A})(25 \Omega) = 30 \text{ V}$$

$$V_{cb} = -IR_1 = -(1.2 \text{ A})(20 \Omega) = -24 \text{ V}$$

$$V_c = E_1 = -19 \text{ V}$$

EXAMPLE

EXAMPLE 5.20 For the network of Fig. 5.50:

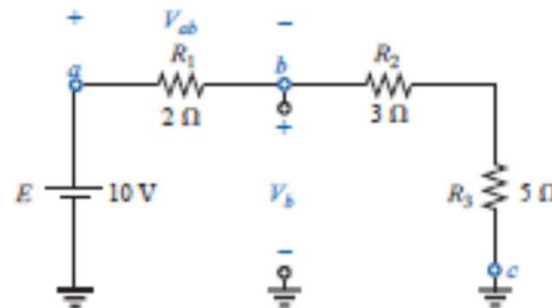


FIG. 5.50
Example 5.20.

- Calculate V_{ab} .
- Determine V_b .
- Calculate V_c .

Solutions:

- a. Voltage divider rule:

$$V_{ab} = \frac{R_1 E}{R_T} = \frac{(2 \Omega)(10 \text{ V})}{2 \Omega + 3 \Omega + 5 \Omega} = +2 \text{ V}$$

- b. Voltage divider rule:

$$V_b = V_{R_2} + V_{R_3} = \frac{(R_2 + R_3)E}{R_T} = \frac{(3 \Omega + 5 \Omega)(10 \text{ V})}{10 \Omega} = 8 \text{ V}$$

$$\text{or } V_b = V_a - V_{ab} = E - V_{ab} = 10 \text{ V} - 2 \text{ V} = 8 \text{ V}$$

- c. $V_c = \text{ground potential} = 0 \text{ V}$