


# EEE 141 ELECTRICAL CIRCUITS

Dr. Shaikh Asif Mahmood  
Associate professor, BUET

Adjunct Faculty, ECE, NSU



# CAPACITORS

Transient



Charging

Discharging

Series and Parallel Capacitors
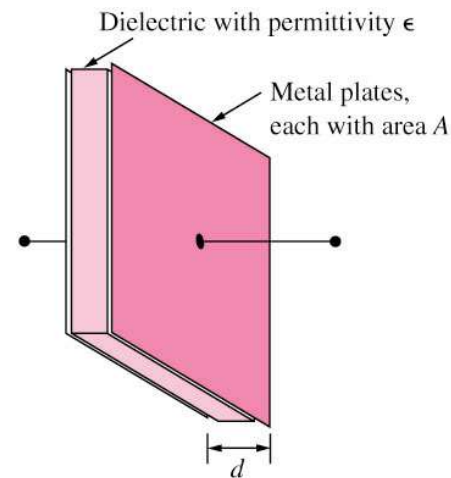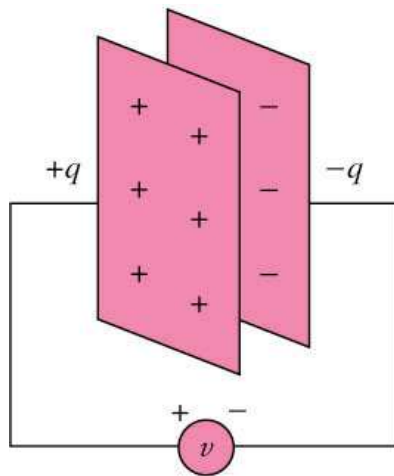
# CAPACITORS


A capacitor is a passive element designed to **store energy** in its **electric field**.



- A **capacitor** consists of two conducting plates separated by an insulator (or dielectric).
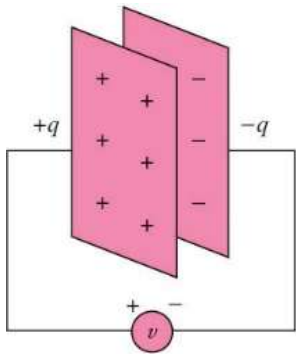
# CAPACITORS

**Capacitance**  $C$  is the ratio of the charge  $q$  on one plate of a capacitor to the voltage difference  $v$  between the two plates, measured in farads (F).




$$q = C v \quad \text{and}$$

$$C = \frac{\varepsilon A}{d}$$

- Where  $\varepsilon$  is the permittivity of the dielectric material between the plates,  $A$  is the surface area of each plate,  $d$  is the distance between the plates.
- Unit: F, pF ( $10^{-12}$ ), nF ( $10^{-9}$ ), and  $\mu\text{F}$  ( $10^{-6}$ )

# TRANSIENTS IN CAPACITIVE NETWORKS: CHARGING PHASE

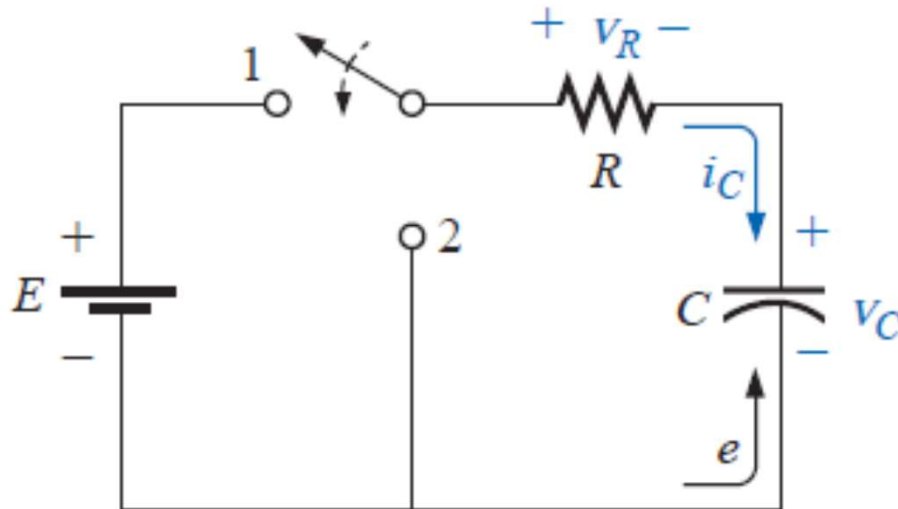


**FIG. 10.24**

*Basic charging network.*

# CHARGING PHASE


- At the instant the switch is closed, electrons are drawn from the top plate and deposited on the bottom plate by the battery, resulting in a net positive charge on the top plate and a negative charge on the bottom plate.
- The transfer of electrons is very rapid at first, slowing down as the potential across the capacitor approaches the applied voltage of the battery.
- When the voltage across the capacitor equals the battery voltage, the transfer of electrons will cease and the plates will have a net charge determined by  $Q = CV_C = CE$ .

# CHARGING PHASE

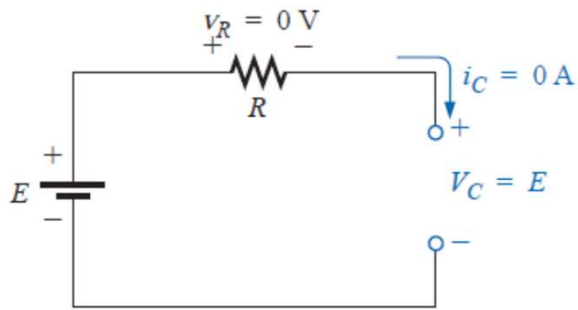


**FIG. 10.27**

*Open-circuit equivalent for a capacitor following the charging phase.*

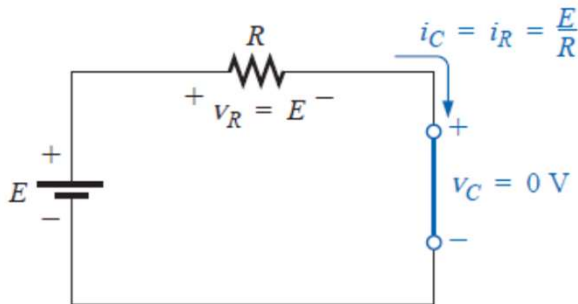


**FIG. 10.28**

*Short-circuit equivalent for a capacitor (switch closed,  $t = 0$ ).*

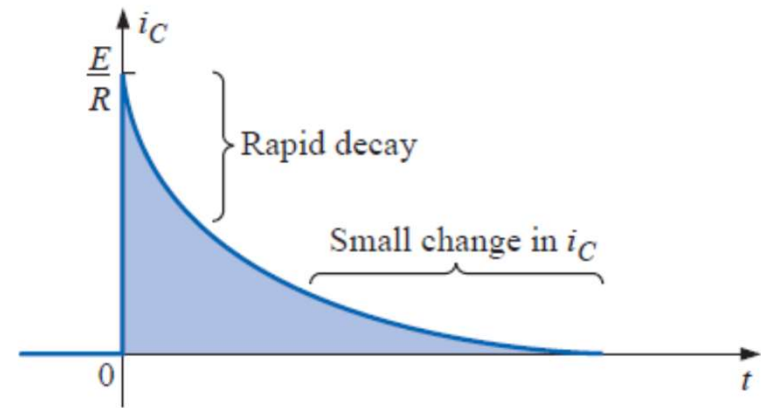

**FIG. 10.25**

*$i_C$  during the charging phase.*

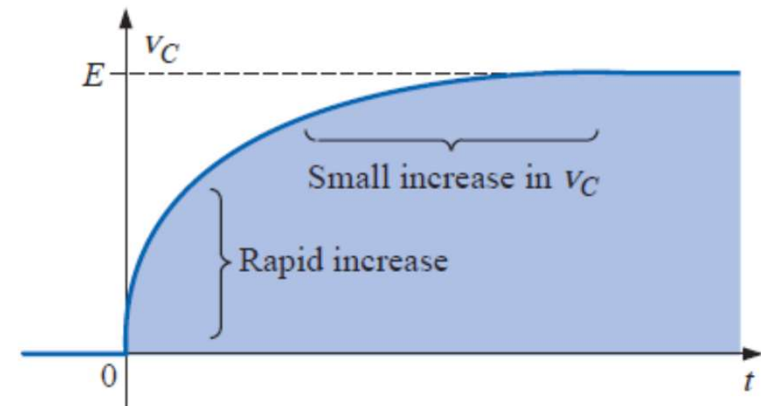

**FIG. 10.26**

*$v_C$  during the charging phase.*

# CHARGING PHASE

***A capacitor can be replaced by an open-circuit equivalent once the charging phase in a dc network has passed.***

$$i_C = \frac{E}{R} e^{-t/RC}$$

***The factor  $RC$  is called the time constant.***



# TIME CONSTANT

$$RC = \left(\frac{V}{I}\right)\left(\frac{Q}{V}\right) = \left(\frac{V}{Q/t}\right)\left(\frac{Q}{V}\right) = t$$

Its symbol is the Greek letter  $\tau$  (tau), and its unit of measure is the second. Thus,

$$\boxed{\tau = RC} \quad (\text{seconds, s}) \quad (10.14)$$

If we substitute  $\tau = RC$  into the exponential function  $e^{-t/RC}$ , we obtain  $e^{-t/\tau}$ . In one time constant,  $e^{-t/\tau} = e^{-\tau/\tau} = e^{-1} = 0.3679$ , or the function equals 36.79% of its maximum value of 1. At  $t = 2\tau$ ,  $e^{-t/\tau} = e^{-2\tau/\tau} = e^{-2} = 0.1353$ , and the function has decayed to only 13.53% of

# CAPACITORS


*The current  $i_C$  of a capacitive network is essentially zero after five time constants of the charging phase have passed in a dc network.*

Since  $C$  is usually found in microfarads or picofarads, the time constant  $\tau = RC$  will never be greater than a few seconds unless  $R$  is very large.

Let us now turn our attention to the charging voltage across the capacitor. Through further mathematical analysis, the following equation for the voltage across the capacitor can be determined:

$$v_C = E(1 - e^{-t/RC}) \quad (10.15)$$

## EXAMPLE

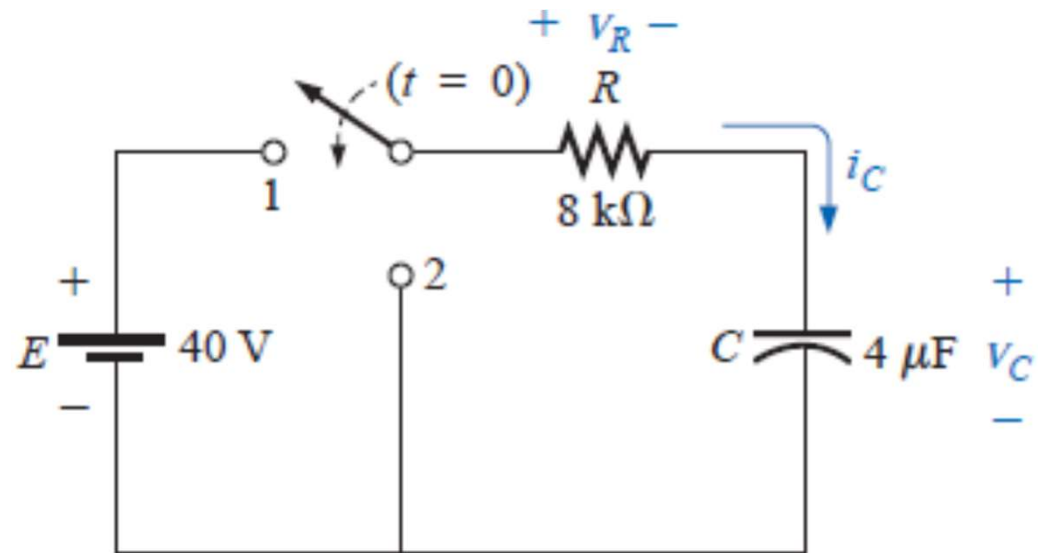

- Find the mathematical expressions for the transient behavior of  $v_C$ ,  $i_C$ , and  $v_R$  for the circuit of Fig. 10.35 when the switch is moved to position 1. Plot the curves of  $v_C$ ,  $i_C$ , and  $v_R$ .
- How much time must pass before it can be assumed, for all practical purposes, that  $i_C \cong 0$  A and  $v_C \cong E$  volts?

### **Solutions:**

a.  $\tau = RC = (8 \times 10^3 \Omega)(4 \times 10^{-6} \text{ F}) = 32 \times 10^{-3} \text{ s} = \mathbf{32 \text{ ms}}$

By Eq. (10.15),

$$v_C = E(1 - e^{-t/\tau}) = \mathbf{40(1 - e^{-t/(32 \times 10^{-3})})}$$

## EXAMPLE

$$\begin{aligned} i_C &= \frac{E}{R} e^{-t/\tau} = \frac{40 \text{ V}}{8 \text{ k}\Omega} e^{-t/(32 \times 10^{-3})} \\ &= (5 \times 10^{-3}) e^{-t/(32 \times 10^{-3})} \end{aligned}$$

By Eq. (10.17),

$$V_R = E e^{-t/\tau} = 40 e^{-t/(32 \times 10^{-3})}$$


The curves appear in Fig. 10.36.

b.  $5\tau = 5(32 \text{ ms}) = 160 \text{ ms}$

# DISCHARGING

$$V_C = Ee^{-t/RC}$$

*discharging*

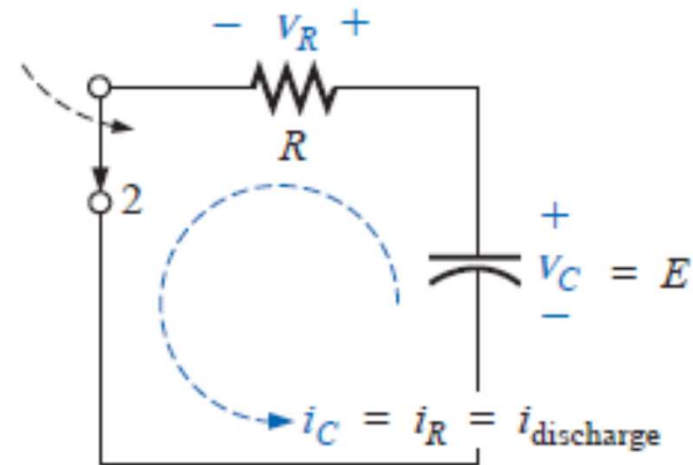

**FIG. 10.38**

*Demonstrating the discharge behavior of a capacitive network.*

$$i_C = \frac{E}{R}e^{-t/RC}$$


*discharging*

The voltage  $V_R = V_C$ , and

$$V_R = Ee^{-t/RC}$$

*discharging*

## EXAMPLE

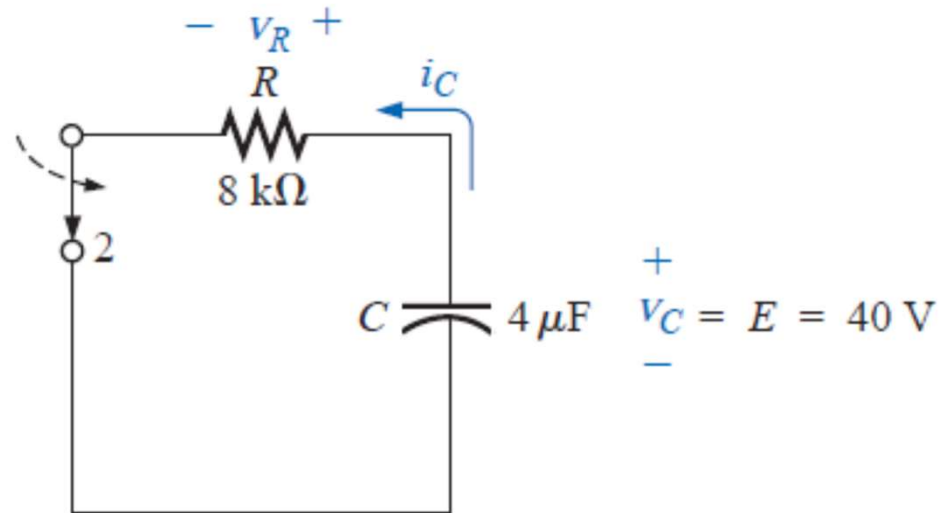

**EXAMPLE 10.6** After  $v_C$  in Example 10.5 has reached its final value of 40 V, the switch is thrown into position 2, as shown in Fig. 10.40. Find the mathematical expressions for the transient behavior of  $v_C$ ,  $i_C$ , and  $v_R$  after the closing of the switch. Plot the curves for  $v_C$ ,  $i_C$ , and  $v_R$  using the defined directions and polarities of Fig. 10.35. Assume that  $t = 0$  when the switch is moved to position 2.






# SOLUTION

$$\tau = 32 \text{ ms}$$


$$v_C = E e^{-t/\tau} = 40 e^{-t/(32 \times 10^{-3})}$$

$$i_C = -\frac{E}{R} e^{-t/\tau} = -(5 \times 10^{-3}) e^{-t/(32 \times 10^{-3})}$$
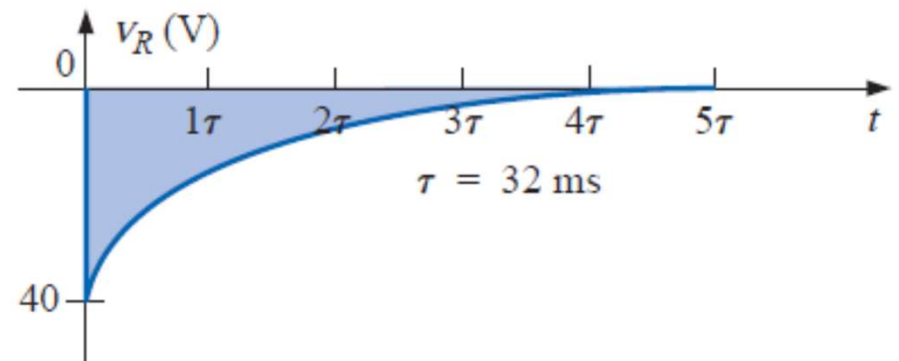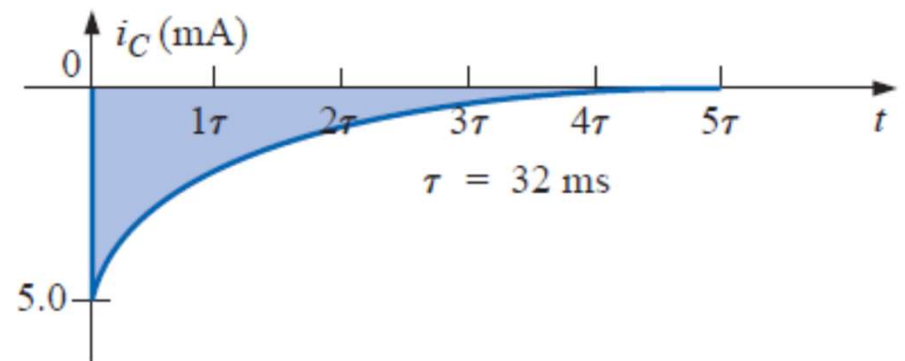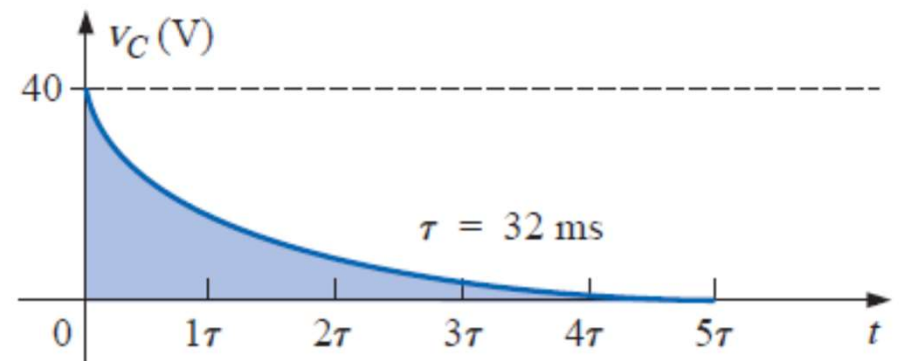
$$v_R = -E e^{-t/\tau} = -40 e^{-t/(32 \times 10^{-3})}$$



## EXAMPLE

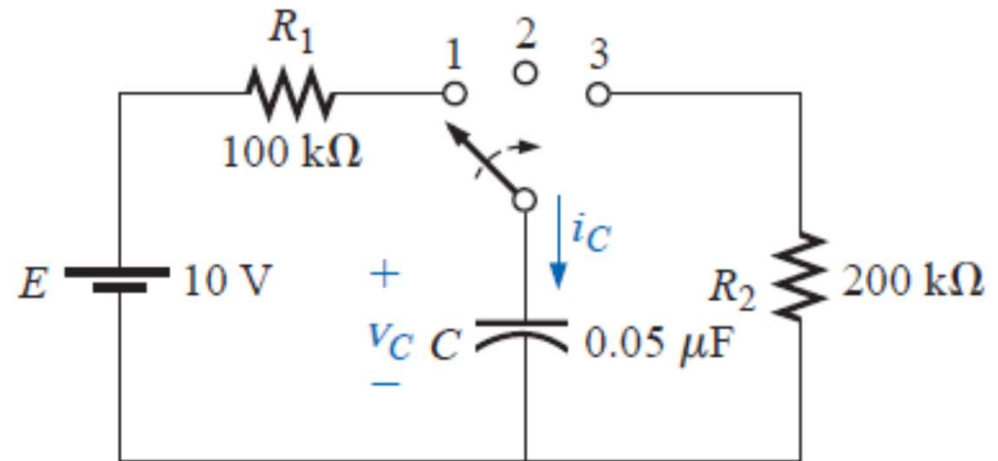

- Find the mathematical expression for the transient behavior of the voltage across the capacitor of Fig. 10.42 if the switch is thrown into position 1 at  $t = 0$  s.
- Repeat part (a) for  $i_C$ .
- Find the mathematical expressions for the response of  $v_C$  and  $i_C$  if the switch is thrown into position 2 at 30 ms (assuming that the leakage resistance of the capacitor is infinite ohms).
- Find the mathematical expressions for the voltage  $v_C$  and current  $i_C$  if the switch is thrown into position 3 at  $t = 48$  ms.
- Plot the waveforms obtained in parts (a) through (d) on the same time axis for the voltage  $v_C$  and the current  $i_C$  using the defined polarity and current direction of Fig. 10.42.



# SOLUTION

a. *Charging phase:*

$$v_C = E(1 - e^{-t/\tau})$$

$$\begin{aligned}\tau &= R_1 C = (100 \times 10^3 \Omega)(0.05 \times 10^{-6} \text{ F}) = 5 \times 10^{-3} \text{ s} \\ &= 5 \text{ ms}\end{aligned}$$

$$v_C = \mathbf{10(1 - e^{-t/(5 \times 10^{-3})})}$$

b.  $i_C = \frac{E}{R_1} e^{-t/\tau}$

$$= \frac{10 \text{ V}}{100 \times 10^3 \Omega} e^{-t/(5 \times 10^{-3})}$$

$$i_C = \mathbf{(0.1 \times 10^{-3})e^{-t/(5 \times 10^{-3})}}$$

c. *Storage phase:*

$$v_C = E = \mathbf{10 \text{ V}}$$

$$i_C = \mathbf{0 \text{ A}}$$

# SOLUTION

d. *Discharge phase* (starting at 48 ms with  $t = 0$  s for the following equations):

$$v_C = Ee^{-t/\tau'}$$


$$\begin{aligned}\tau' &= R_2C = (200 \times 10^3 \Omega)(0.05 \times 10^{-6} \text{ F}) = 10 \times 10^{-3} \text{ s} \\ &= 10 \text{ ms}\end{aligned}$$

$$v_C = \mathbf{10e^{-t/(10 \times 10^{-3})}}$$

$$\begin{aligned}i_C &= -\frac{E}{R_2}e^{-t/\tau'} \\ &= -\frac{10 \text{ V}}{200 \times 10^3 \Omega}e^{-t/(10 \times 10^{-3})}\end{aligned}$$

$$i_C = \mathbf{-(0.05 \times 10^{-3})e^{-t/(10 \times 10^{-3})}}$$


# SOLUTION

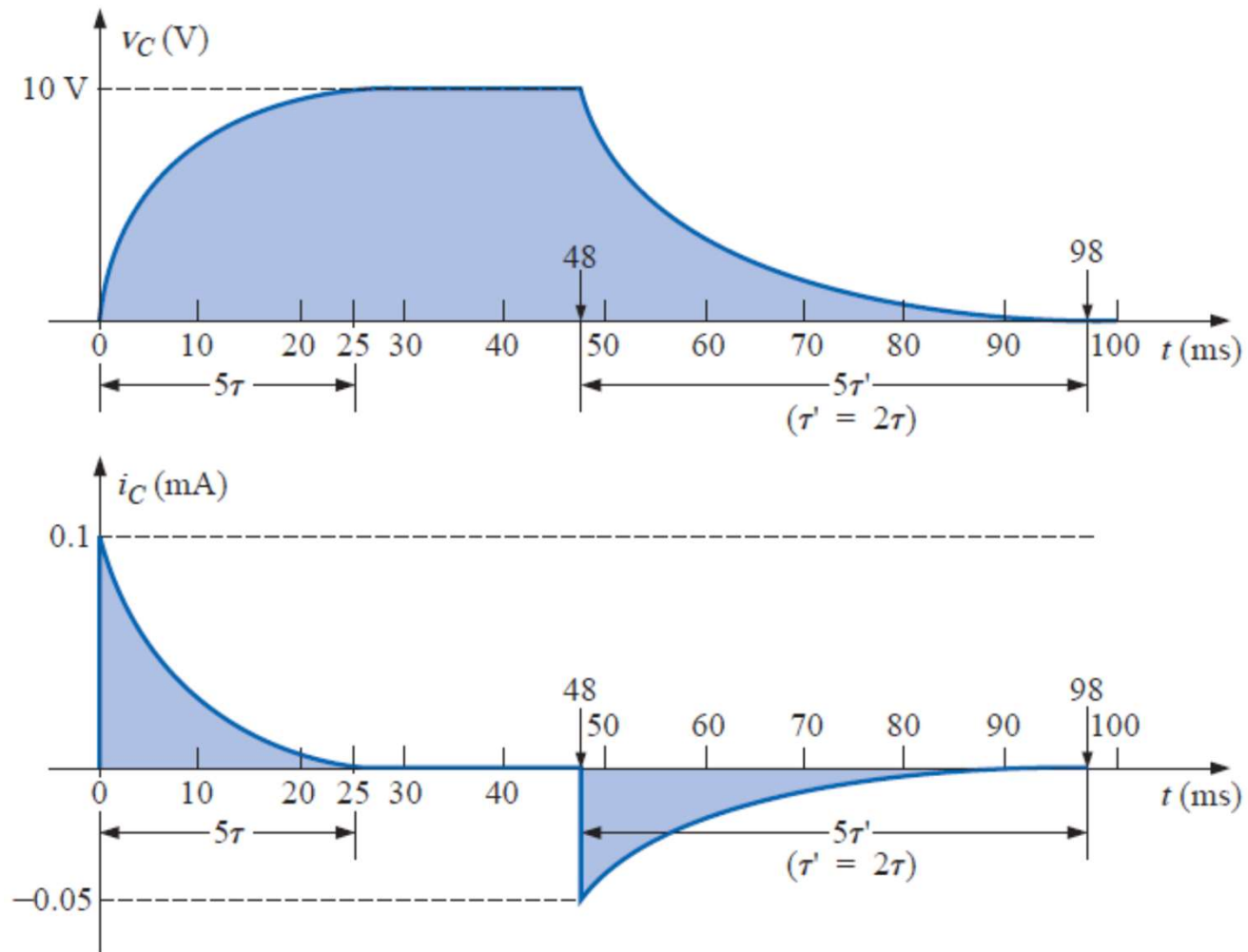
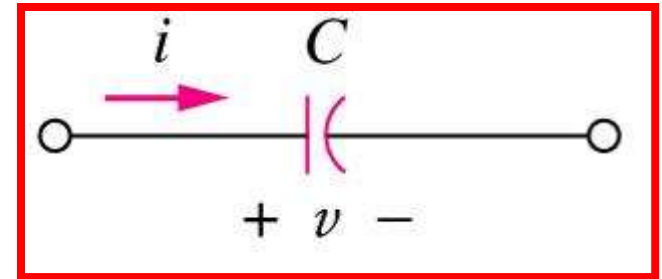
# CAPACITORS

If  $i$  is flowing into the +ve terminal of  $C$

- Charging  $\Rightarrow i$  is +ve
- Discharging  $\Rightarrow i$  is -ve



- The current-voltage relationship of capacitor according to above convention is

$$i = C \frac{d v}{d t}$$


and

$$v = \frac{1}{C} \int_{t_0}^t i d t + v(t_0)$$

# CAPACITORS

The energy, **w**, stored in the capacitor is



$$w = \frac{1}{2} C v^2$$

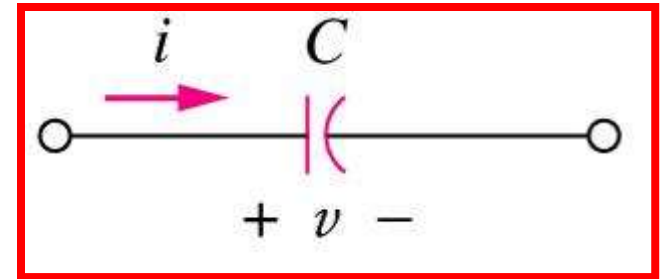

- A capacitor is
  - an **open circuit** to dc ( $dv/dt = 0$ ).
  - its voltage **cannot change abruptly**.
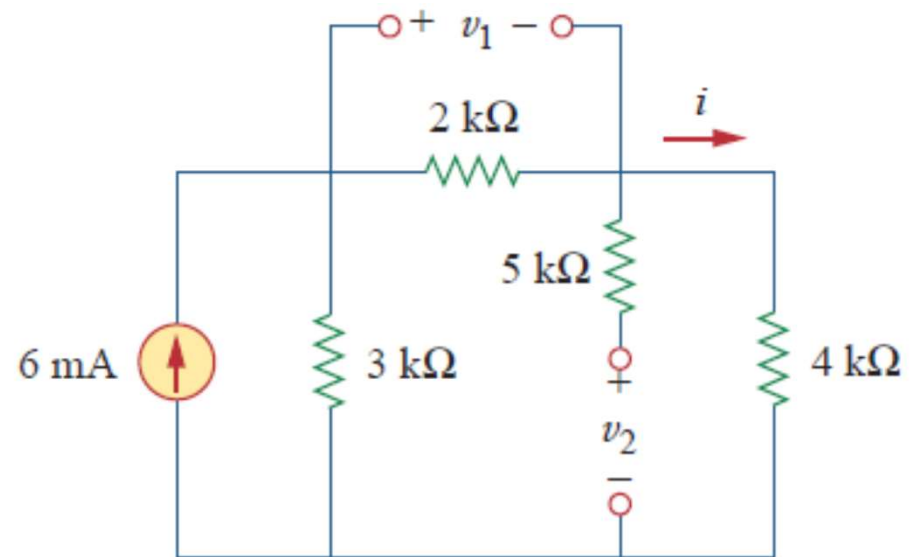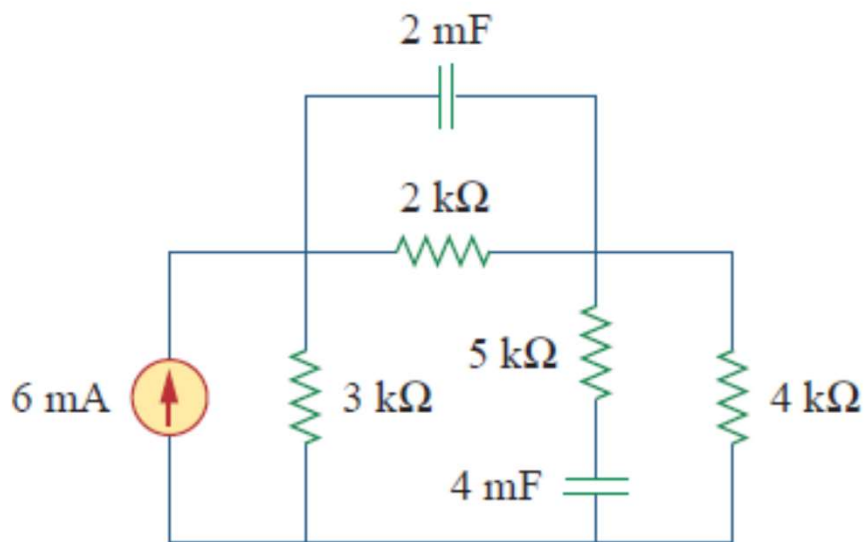
# EXAMPLE

Obtain the energy stored in each capacitor under dc conditions.



## SOLUTION

$$i = \frac{3}{3 + 2 + 4}(6 \text{ mA}) = 2 \text{ mA}$$

Hence, the voltages  $v_1$  and  $v_2$  across the capacitors are

$$v_1 = 2000i = 4 \text{ V} \quad v_2 = 4000i = 8 \text{ V}$$


and the energies stored in them are

$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(2 \times 10^{-3})(4)^2 = 16 \text{ mJ}$$


$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(4 \times 10^{-3})(8)^2 = 128 \text{ mJ}$$
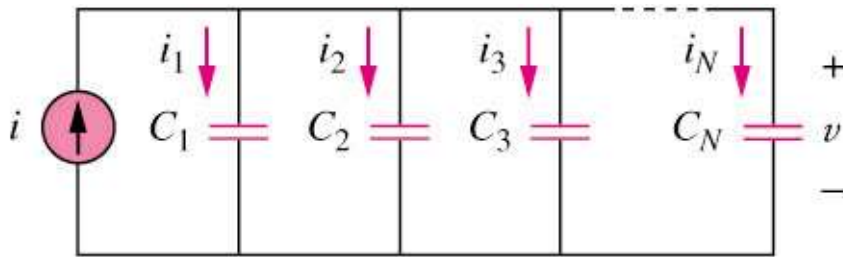
# SERIES AND PARALLEL CAPACITORS

The equivalent capacitance of  $N$  **parallel-connected** capacitors is the sum of the individual capacitances.



(a)

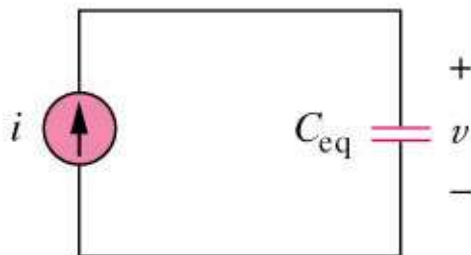


(b)

$$C_{eq} = C_1 + C_2 + \dots + C_N$$



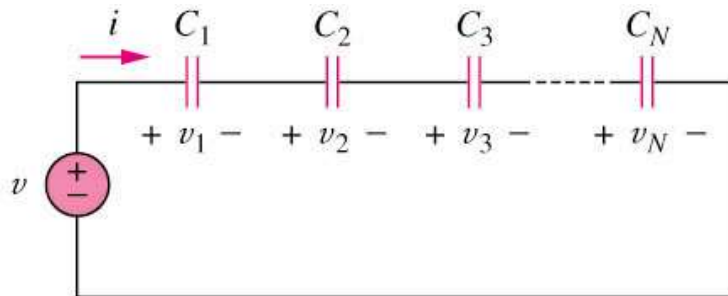
## SERIES AND PARALLEL CAPACITORS

The equivalent capacitance of  $N$  **series-connected** capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.



(a)

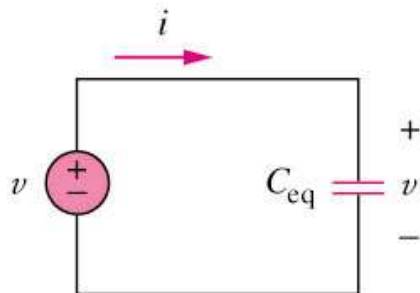
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$



(b)
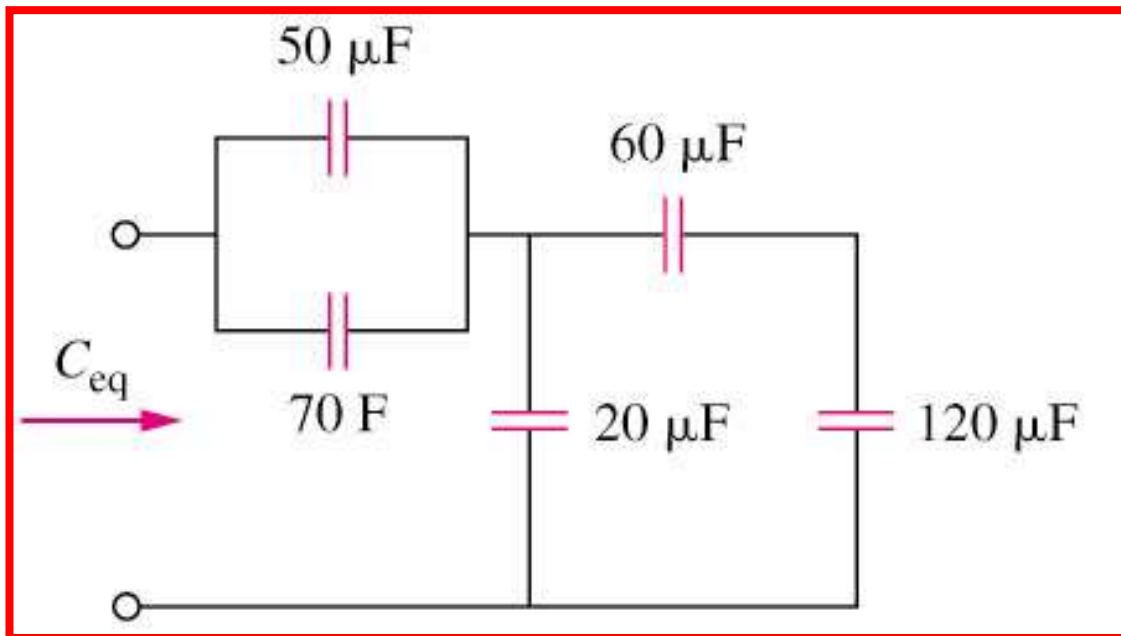
## SERIES AND PARALLEL CAPACITORS (EXAMPLE)


Find the equivalent capacitance seen at the terminals of the circuit in the circuit shown below:



**Answer:**

$$C_{eq} = \underline{40\ \mu\text{F}}$$

## EXAMPLE

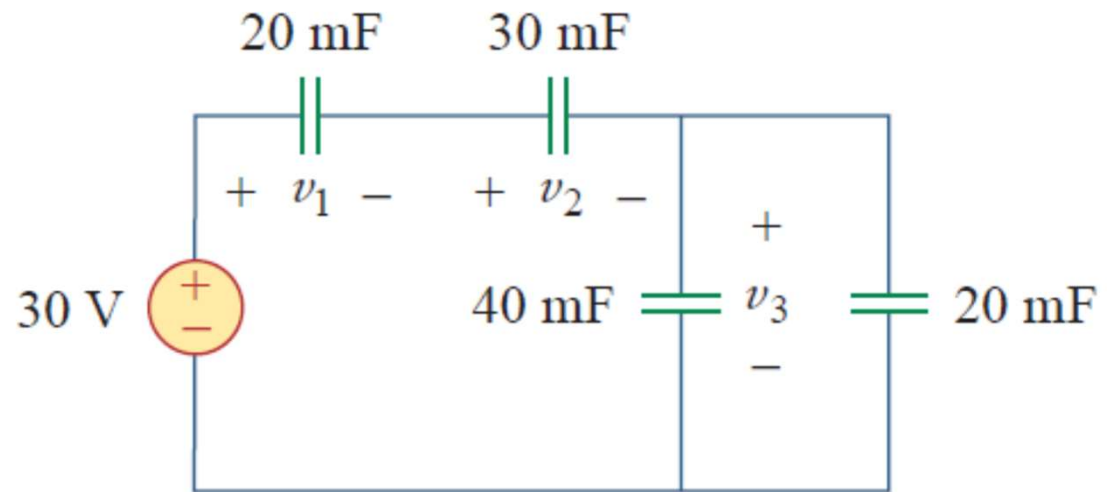

$$C_{\text{eq}} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} \text{ mF} = 10 \text{ mF}$$

The total charge is

$$q = C_{\text{eq}}v = 10 \times 10^{-3} \times 30 = 0.3 \text{ C}$$

## EXAMPLE

This is the charge on the 20-mF and 30-mF capacitors, because they are in series with the 30-V source. (A crude way to see this is to imagine that charge acts like current, since  $i = dq/dt$ .) Therefore,

$$v_1 = \frac{q}{C_1} = \frac{0.3}{20 \times 10^{-3}} = 15 \text{ V} \quad v_2 = \frac{q}{C_2} = \frac{0.3}{30 \times 10^{-3}} = 10 \text{ V}$$

Having determined  $v_1$  and  $v_2$ , we now use KVL to determine  $v_3$  by

$$v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$


## EXAMPLE

Alternatively, since the 40-mF and 20-mF capacitors are in parallel, they have the same voltage  $v_3$  and their combined capacitance is  $40 + 20 = 60$  mF. This combined capacitance is in series with the 20-mF and 30-mF capacitors and consequently has the same charge on it. Hence,

$$v_3 = \frac{q}{60 \text{ mF}} = \frac{0.3}{60 \times 10^{-3}} = 5 \text{ V}$$
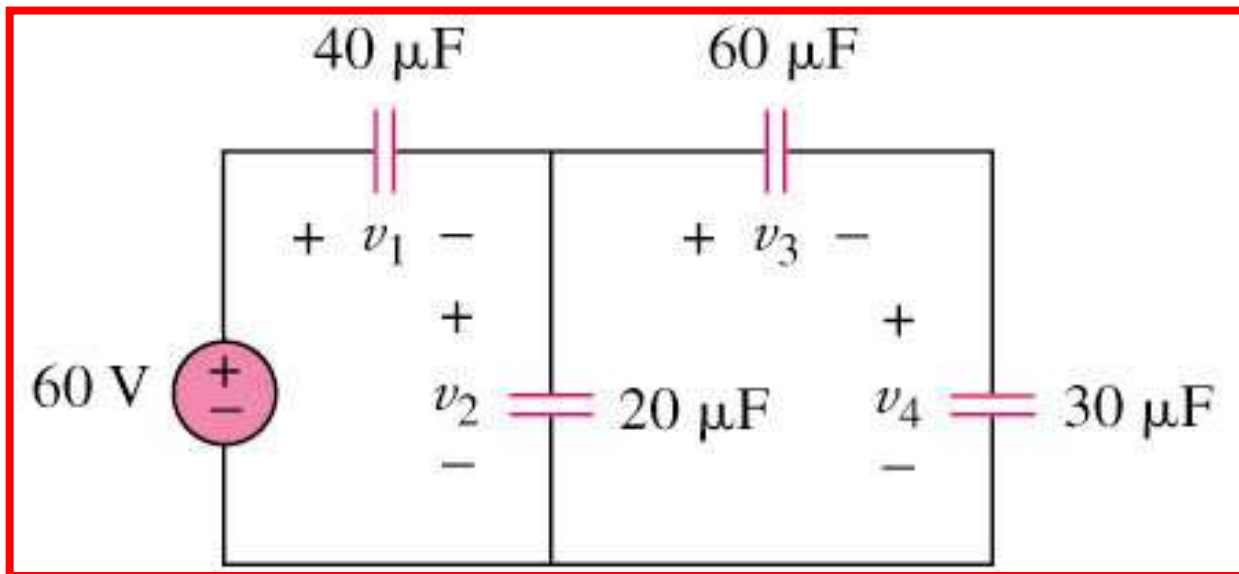
## SERIES AND PARALLEL CAPACITORS (EXAMPLE)

Find the voltage across each of the capacitors in the circuit shown below:



**Answer:**

$$v_1 = 30\text{V}$$

$$v_2 = 30\text{V}$$

$$v_3 = 10\text{V}$$

$$v_4 = 20\text{V}$$