


# EEE 141 ELECTRICAL CIRCUITS

Dr. Shaikh Asif Mahmood  
Associate professor, BUET

Adjunct Faculty, ECE, NSU



# METHODS OF ANALYSIS

Source Conversion.

Branch Current Analysis.

Mesh Analysis.

Nodal Analysis.

# INTRODUCTION

The steps shown in the previous chapters cannot be applied if the sources are not in series or parallel.

Other methods have been developed to solve network with any arrangement of sources.

These methods apply also for single source network,

These methods are:

**1- Branch-current analysis**

**2- Mesh analysis**

**3- Nodal analysis**

Any of these method can be applied, the best method cannot be defined.

All the methods can be applied to **linear bilateral** networks.

**Linear**  $\equiv$  elements of the network are independent of the voltage applied across or the current through them,

**Bilateral**  $\equiv$  no change in the behavior if current or voltage is reversed.


# CURRENT SOURCES

Current source is the dual of the voltage source:

Current source supplies fixed current to the branch in which it is located; the voltage across its terminal can vary.

The interest in current source is due to semiconductor devices (transistors),

## Current-controlled devices

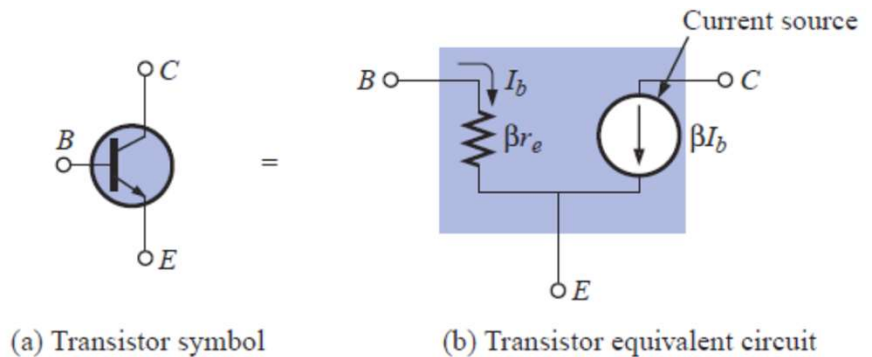

**FIG. 8.1**


*Current source within the transistor equivalent circuit.*

Transistor behaves like a current source.

Symbol of current source  $\equiv$  circle with an arrow.

Arrow indicates the direction of current supplied.

# IDEAL VOLTAGE AND CURRENT SOURCE

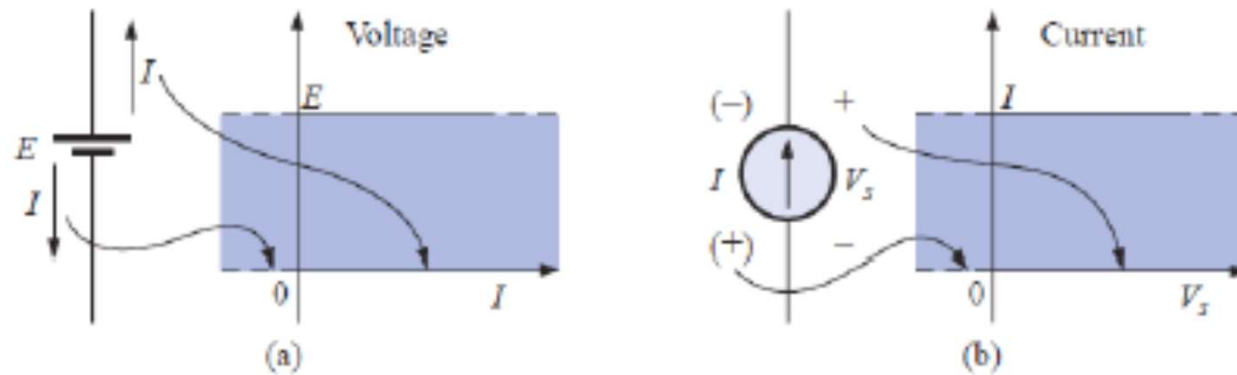

**FIG. 8.2**

*Comparing the characteristics of an ideal voltage and current source.*

- *A current source determines the current in the branch in which it is located*
- *The magnitude and polarity of the voltage across a current source are a function of the network to which it is applied.*

# EXAMPLE

**EXAMPLE 8.2** Find the voltage  $V_s$  and the currents  $I_1$  and  $I_2$  for the network of Fig. 8.4.

**Solution:**

$$V_s = E = 12 \text{ V}$$


$$I_2 = \frac{V_R}{R} = \frac{E}{R} = \frac{12 \text{ V}}{4 \Omega} = 3 \text{ A}$$

Applying Kirchhoff's current law:

$$I = I_1 + I_2$$

and

$$I_1 = I - I_2 = 7 \text{ A} - 3 \text{ A} = 4 \text{ A}$$

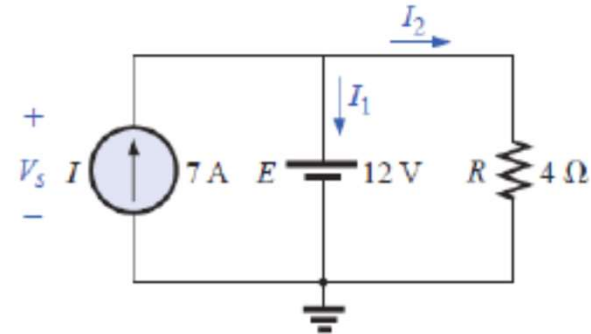

**EXAMPLE 8.3** Determine the current  $I_1$  and the voltage  $V_s$  for the network of Fig. 8.5.

**Solution:** Using the current divider rule:

$$I_1 = \frac{R_2 I}{R_2 + R_1} = \frac{(1 \Omega)(6 \text{ A})}{1 \Omega + 2 \Omega} = 2 \text{ A}$$

The voltage  $V_1$  is

$$V_1 = I_1 R_1 = (2 \text{ A})(2 \Omega) = 4 \text{ V}$$


and, applying Kirchhoff's voltage law,

$$+V_s - V_1 - 20 \text{ V} = 0$$

and

$$\begin{aligned} V_s &= V_1 + 20 \text{ V} = 4 \text{ V} + 20 \text{ V} \\ &= \mathbf{24 \text{ V}} \end{aligned}$$

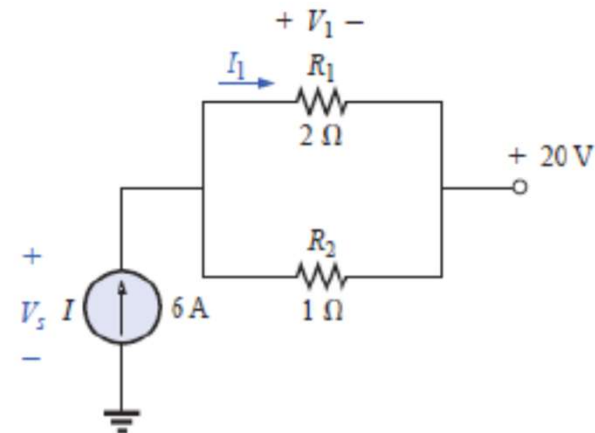Note the polarity of  $V_s$  as determined by the multisource network.



# SOURCE CONVERSIONS

The current (voltage) source described are *ideal sources*  $\Rightarrow$  No internal resistance  
Real sources ( voltage or current) have *internal resistance*

Real Voltage source:

- $E \equiv$  voltage source rating
- $R_s \equiv$  internal resistance (series)

$R_s = 0$  (much smaller than any series resistor)  
 $\Rightarrow$  **Ideal voltage source**

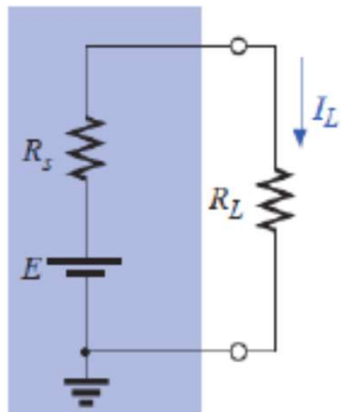


FIG. 8.6

Practical voltage source.

$$I_L = \frac{E}{R_s + R_L}$$

Real Current source:

- $I \equiv$  current source rating
- $R_s \equiv$  internal resistance ( parallel )

$R_s = \infty$  (much larger than any parallel resistor)  
 $\Rightarrow$  **Ideal Current source**

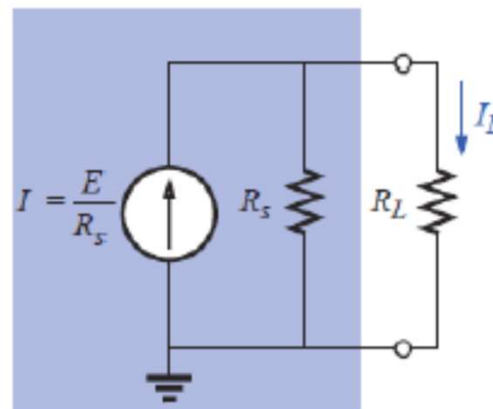


FIG. 8.7

Practical current source.

$$I_L = \frac{R_s \cdot I}{R_s + R_L}$$

# SOURCE CONVERSIONS

Sources with their internal resistance included can be converted from one type to the other type.


*Source conversions are equivalent only at their external terminals.*

➤  $R_s$  is the same (position changed)

➤  $E = I \cdot R_s$

As far as terminal point (a) and (b) and the circuit in between there is no difference:

- Same current
- Same voltage
- Same power

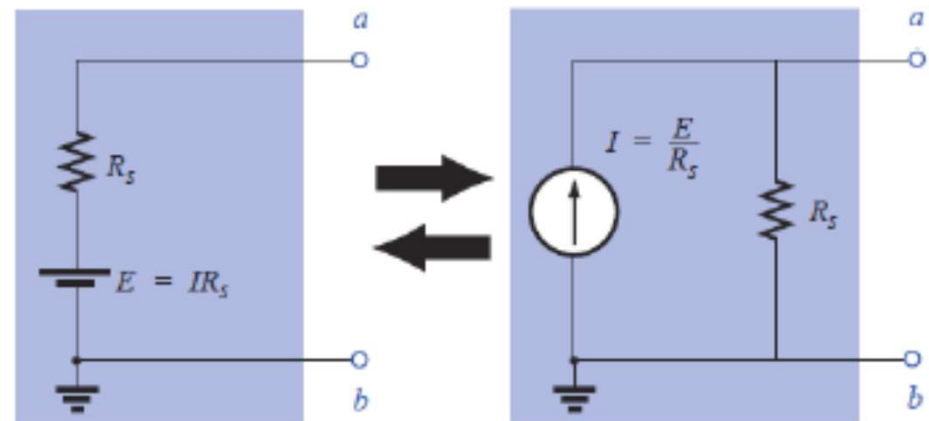

**FIG. 8.8**

*Source conversion.*



# EXAMPLE

## EXAMPLE 8.4

- Convert the voltage source of Fig. 8.9(a) to a current source, and calculate the current through the  $4\text{-}\Omega$  load for each source.
- Replace the  $4\text{-}\Omega$  load with a  $1\text{-k}\Omega$  load, and calculate the current  $I_L$  for the voltage source.
- Repeat the calculation of part (b) assuming that the voltage source is ideal ( $R_s = 0\text{ }\Omega$ ) because  $R_L$  is so much larger than  $R_s$ . Is this one of those situations where assuming that the source is ideal is an appropriate approximation?

### Solutions:

- See Fig. 8.9.


$$\text{Fig. 8.9(a): } I_L = \frac{E}{R_s + R_L} = \frac{6\text{ V}}{2\text{ }\Omega + 4\text{ }\Omega} = 1\text{ A}$$

$$\text{Fig. 8.9(b): } I_L = \frac{R_s I}{R_s + R_L} = \frac{(2\text{ }\Omega)(3\text{ A})}{2\text{ }\Omega + 4\text{ }\Omega} = 1\text{ A}$$

$$\text{b. } I_L = \frac{E}{R_s + R_L} = \frac{6\text{ V}}{2\text{ }\Omega + 1\text{ k}\Omega} \cong 5.99\text{ mA}$$

$$\text{c. } I_L = \frac{E}{R_L} = \frac{6\text{ V}}{1\text{ k}\Omega} = 6\text{ mA} \cong 5.99\text{ mA}$$

Yes,  $R_L \gg R_s$  (voltage source).

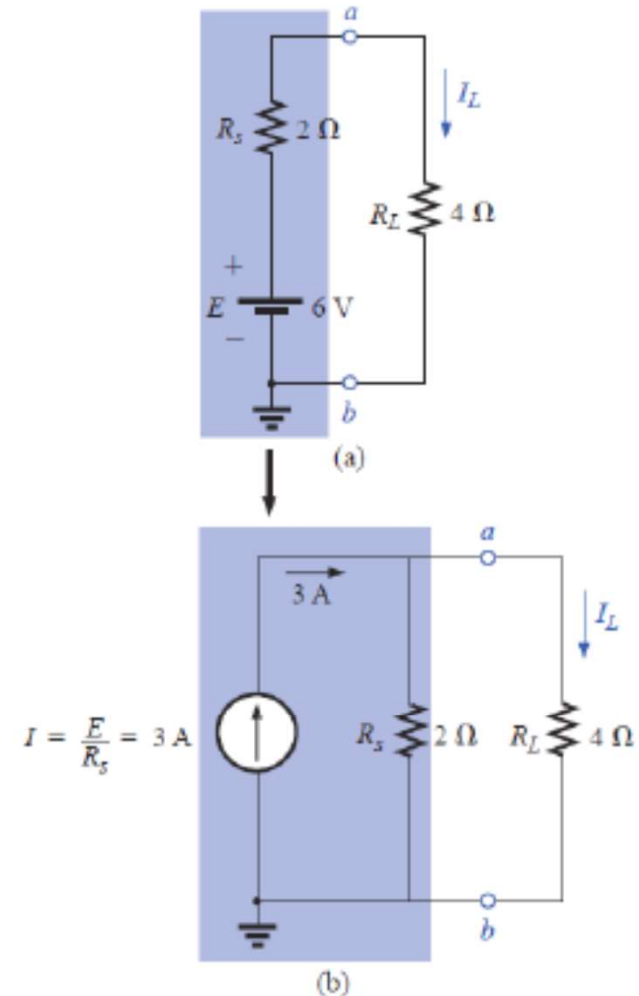

# EXAMPLE

## EXAMPLE 8.5

- Convert the current source of Fig. 8.10(a) to a voltage source, and find the load current for each source.
- Replace the 6-k $\Omega$  load with a 10- $\Omega$  load, and calculate the current  $I_L$  for the current source.
- Repeat the calculation of part (b) assuming that the current source is ideal ( $R_s = \infty \Omega$ ) because  $R_L$  is so much smaller than  $R_s$ . Is this one of those situations where assuming that the source is ideal is an appropriate approximation?

### Solutions:

- See Fig. 8.10.


$$\text{Fig. 8.10(a): } I_L = \frac{R_s I}{R_s + R_L} = \frac{(3 \text{ k}\Omega)(9 \text{ mA})}{3 \text{ k}\Omega + 6 \text{ k}\Omega} = \mathbf{3 \text{ mA}}$$

$$\text{Fig. 8.10(b): } I_L = \frac{E}{R_s + R_L} = \frac{27 \text{ V}}{3 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{27 \text{ V}}{9 \text{ k}\Omega} = \mathbf{3 \text{ mA}}$$


$$\text{b. } I_L = \frac{R_s I}{R_s + R_L} = \frac{(3 \text{ k}\Omega)(9 \text{ mA})}{3 \text{ k}\Omega + 10 \Omega} = \mathbf{8.97 \text{ mA}}$$

$$\text{c. } I_L = I = \mathbf{9 \text{ mA}} \cong 8.97 \text{ mA}$$

Yes,  $R_s \gg R_L$  (current source).

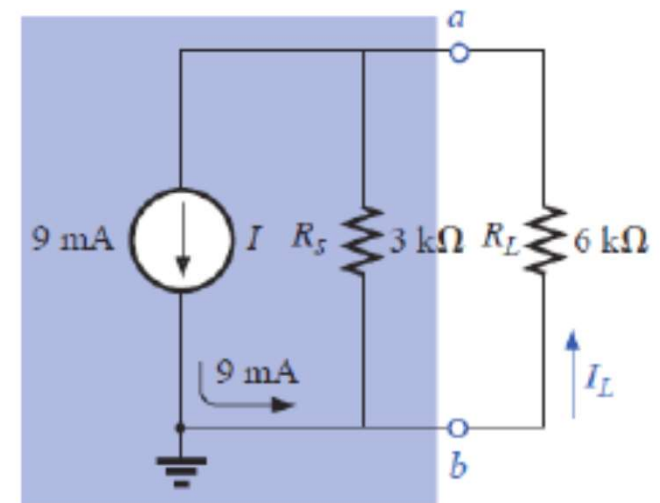

(a)

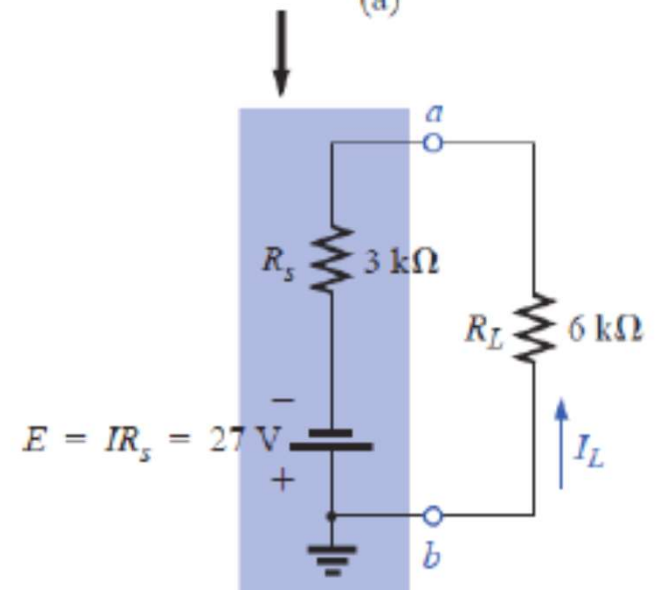

(b)

# CURRENT SOURCES IN PARALLEL



Current sources in parallel: they may all be replaced by one current source having the magnitude and direction of the resultant:

Summing the currents in one direction

Subtracting the sum of the currents in the opposite direction

New parallel resistance is found like any parallel resistors in parallel


# EXAMPLE

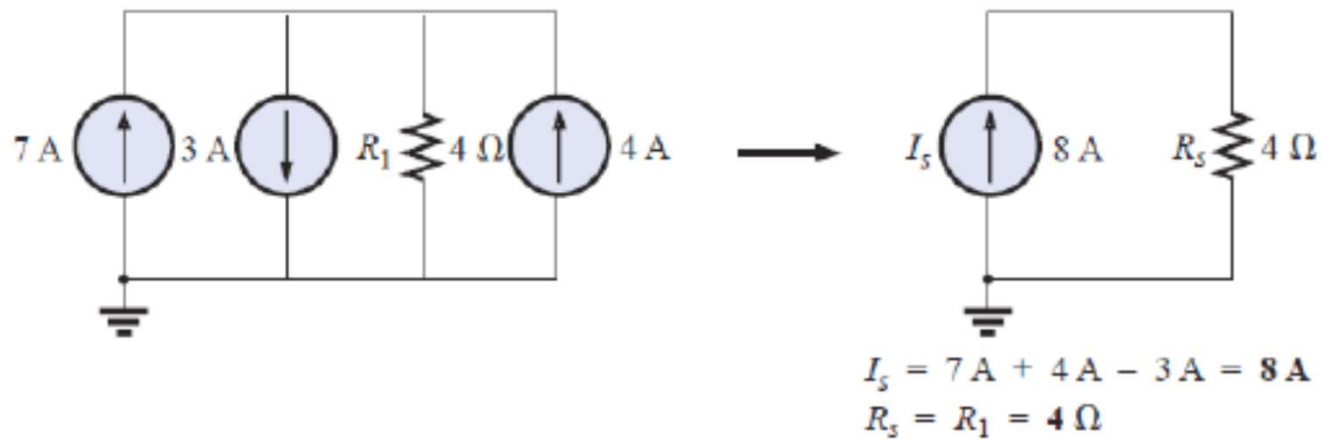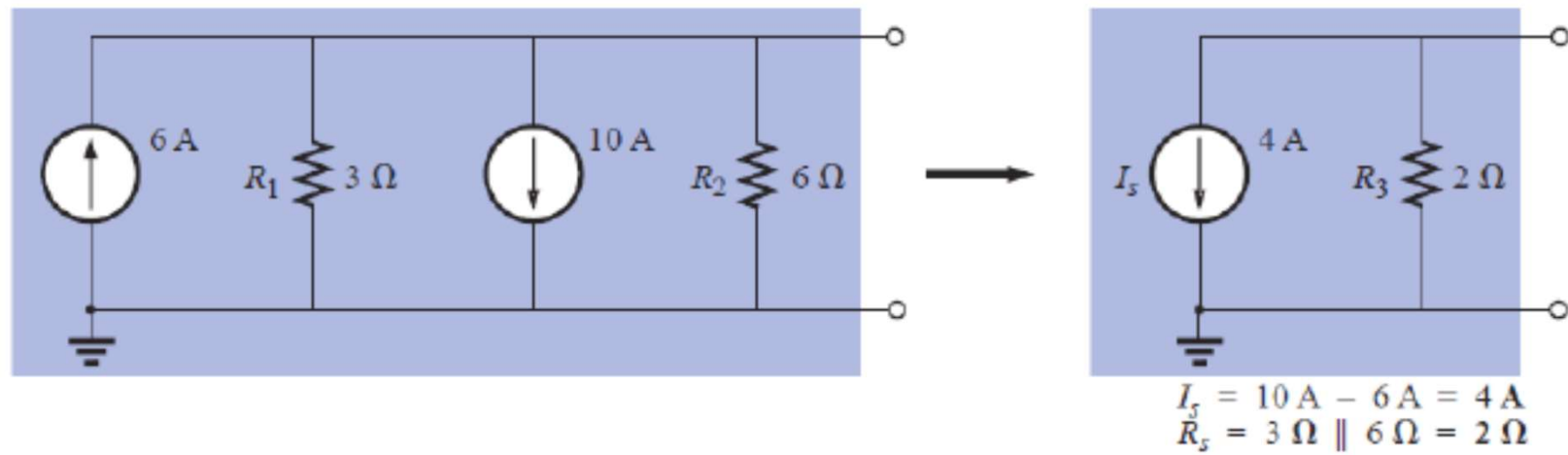

# EXAMPLE

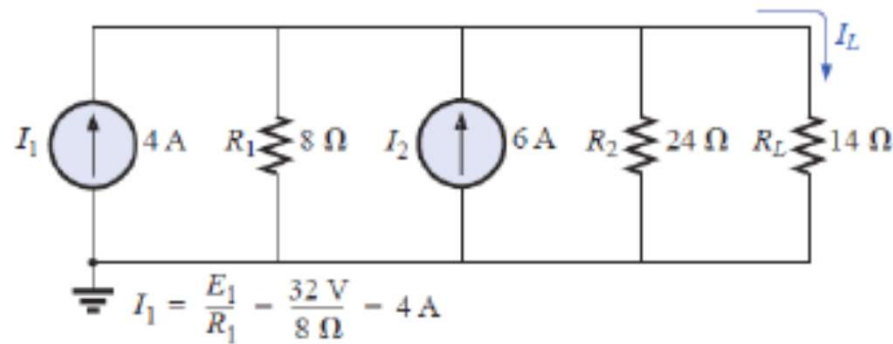**EXAMPLE 8.7** Reduce the network of Fig. 8.13 to a single current source, and calculate the current through  $R_L$ .

**Solution:** In this example, the voltage source will first be converted to a current source as shown in Fig. 8.14. Combining current sources,





$$I_s = I_1 + I_2 = 4 \text{ A} + 6 \text{ A} = 10 \text{ A}$$

and

$$R_s = R_1 \parallel R_2 = 8 \Omega \parallel 24 \Omega = 6 \Omega$$

Applying the current divider rule to the resulting network of Fig. 8.15,

$$I_L = \frac{R_s I_s}{R_s + R_L} = \frac{(6 \Omega)(10 \text{ A})}{6 \Omega + 14 \Omega} = \frac{60 \text{ A}}{20} = 3 \text{ A}$$

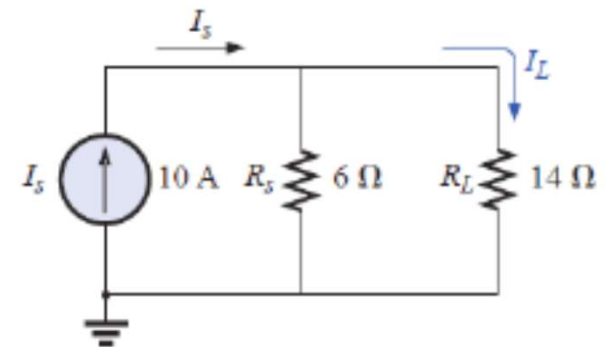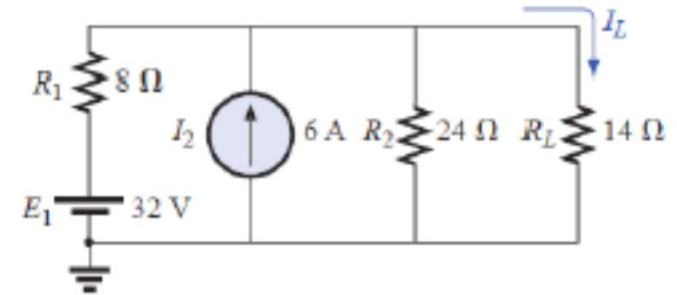


**FIG. 8.15**

Network of Fig. 8.14 reduced to its simplest form.

# CURRENT SOURCES IN SERIES

*current sources of different current ratings are not connected in series,*

Voltage sources of different voltage ratings are not connected in parallel.

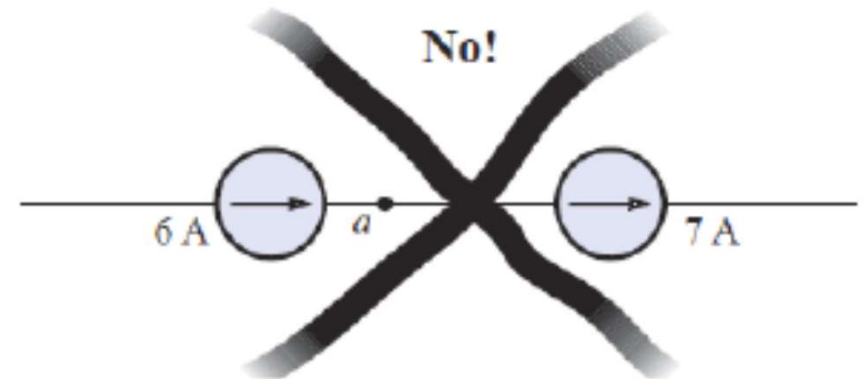

**FIG. 8.18**  
*Invalid situation.*



# MESH ANALYSIS

Mesh  $\equiv$  closed loop (like a fence)

1. Assign a current in clockwise direction to each *independent*, closed loop of the network.

- Not necessarily the clockwise direction.
- Any direction can be chosen ---
- Remaining steps follow the choice properly.

However, by choosing the clockwise direction as a standard, we can develop a shorthand method for writing the required equations that will save time and possibly prevent some common errors.


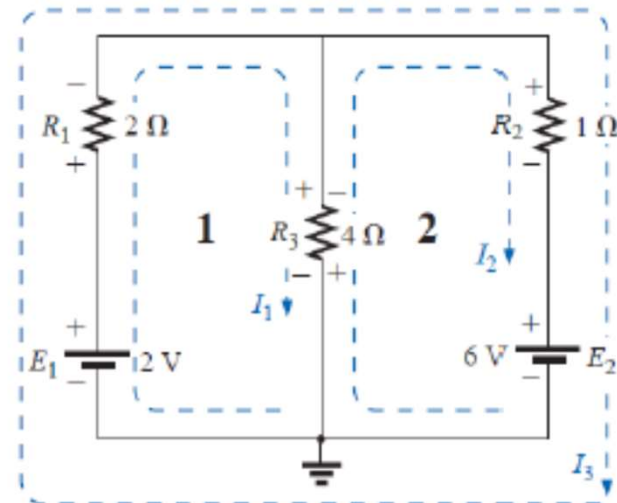
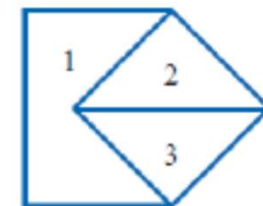


FIG. 8.26

Defining the mesh currents for a "two-window" network.


Independent closed loop

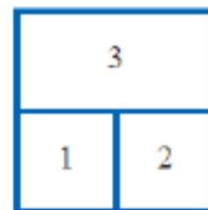

# MESH ANALYSIS

2. *Indicate the polarities within each loop for each resistor as determined by the assumed direction of loop current for that loop.*

*Note the requirement that the polarities be placed within each loop. This requires, as shown in Fig. 8.26, that the  $4\Omega$  resistor have two sets of polarities across it.*

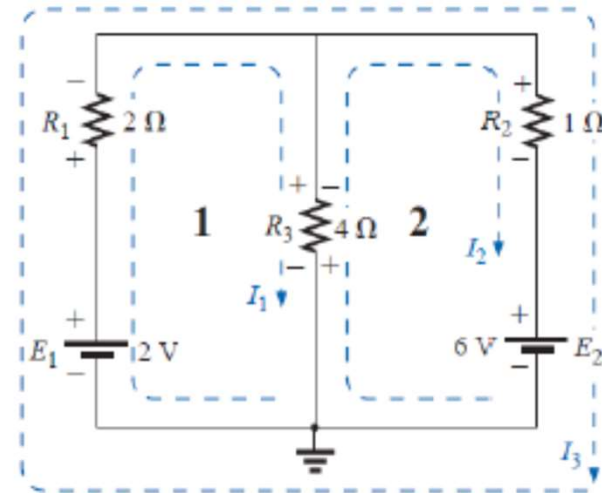


**FIG. 8.26**

*Defining the mesh currents for a "two-window" network.*

3. *Apply Kirchhoff's voltage law around each closed loop.*  
*Again, the clockwise direction is chosen to establish uniformity.*
  - a. *If a resistor has two or more assumed currents through it,*  $I_T = \sum I$
  - b. *The polarity of a voltage source is unaffected by the direction of the assigned loop currents.*
4. *Solve the resulting simultaneous linear equations for the assumed loop currents.*



# EXAMPLE

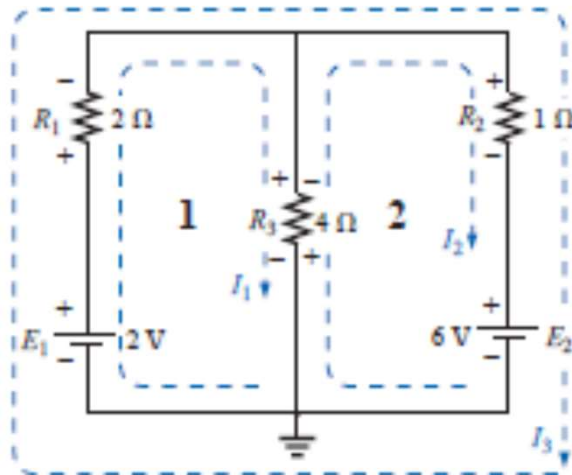

loop 1:  $+E_1 - V_1 - V_3 = 0$  (clockwise starting at point *a*)

$$+2\text{ V} - (2\ \Omega)I_1 - \overbrace{(4\ \Omega)(I_1 - I_2)}^{\substack{\text{Voltage drop across} \\ 4\text{-}\Omega \text{ resistor}}} = 0$$

Subtracted since  $I_2$  is opposite in direction to  $I_1$ .

Total current through 4- $\Omega$  resistor

loop 2:  $-V_3 - V_2 - E_2 = 0$  (clockwise starting at point *b*)

$$-(4\ \Omega)(I_2 - I_1) - (1\ \Omega)I_2 - 6\text{ V} = 0$$

*Step 4:* The equations are then rewritten as follows (without units for clarity):

$$\text{loop 1: } +2 - 2I_1 - 4I_1 + 4I_2 = 0$$

$$\text{loop 2: } -4I_2 + 4I_1 - 1I_2 - 6 = 0$$

and

$$\text{loop 1: } +2 - 6I_1 + 4I_2 = 0$$

$$\text{loop 2: } -5I_2 + 4I_1 - 6 = 0$$

or


$$\text{loop 1: } -6I_1 + 4I_2 = -2$$

$$\text{loop 2: } +4I_1 - 5I_2 = +6$$

Applying determinants will result in

$$I_1 = -1\text{ A} \quad \text{and} \quad I_2 = -2\text{ A}$$

# EXAMPLE

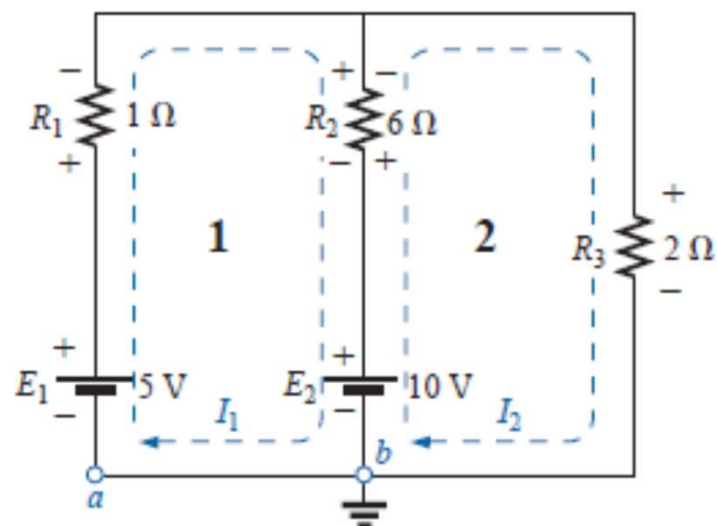

**FIG. 8.27**  
Example 8.12.

loop 1:  $+E_1 - V_1 - V_2 - E_2 = 0$  (clockwise starting at point  $a$ )

$$+5 \text{ V} - (1 \Omega)I_1 - (6 \Omega)(I_1 - I_2) - 10 \text{ V} = 0$$

$I_2$  flows through the 6-Ω resistor  
in the direction opposite to  $I_1$ .

loop 2:  $E_2 - V_2 - V_3 = 0$  (clockwise starting at point  $b$ )

$$+10 \text{ V} - (6 \Omega)(I_2 - I_1) - (2 \Omega)I_2 = 0$$

The equations are rewritten as

$$\left. \begin{array}{l} 5 - I_1 - 6I_1 + 6I_2 - 10 = 0 \\ 10 - 6I_2 + 6I_1 - 2I_2 = 0 \end{array} \right\} \begin{array}{l} -7I_1 + 6I_2 = 5 \\ +6I_1 - 8I_2 = -10 \end{array}$$

Step 4:

$$I_1 = \frac{\begin{vmatrix} 5 & 6 \\ -10 & -8 \end{vmatrix}}{\begin{vmatrix} -7 & 6 \\ 6 & -8 \end{vmatrix}} = \frac{-40 + 60}{56 - 36} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{\begin{vmatrix} -7 & 5 \\ 6 & -10 \end{vmatrix}}{20} = \frac{70 - 30}{20} = \frac{40}{20} = 2 \text{ A}$$