

PHY 108L: Prelab 1


Date:

Name:

Student ID:

These questions need to be completed before starting the lab. Please show all workings.

Question 1: In the circuit shown below, possible positions of a voltmeter and an ammeter are labeled by numbers in circles. What should be the correct location of ammeter and voltmeter to measure the total current and the total voltage respectively?

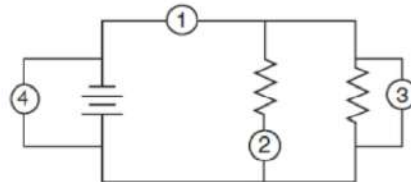

Question 2: Calculate the value of R_1 and R_2 by finding slopes from the given I-V graph.

