

PHY 108L: Prelab 2


Date:

Name:


Student ID:

These questions need to be completed before starting the lab. Please show all workings.

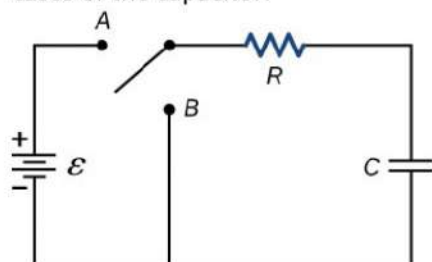
Question 1: A an RC circuit shown in Figure 1(a). Label the Figures 1(b) to show the circuit for charging and discharging cases of the capacitor.



(a) Original circuit

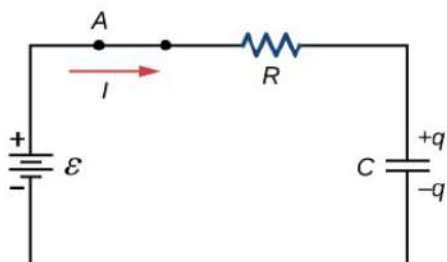

(b)

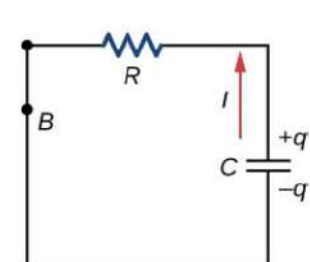

(b)

Question 2: From the following graph, calculate the approximate values of RC time constant when (a) the capacitor is charging and (b) discharging.

