

PHY108L: Prelab 6

Date:


Name:

Student ID:

These questions need to be completed before starting the lab. Please show all workings.

1. Write your understanding on resonance condition for an RLC circuit. What is the reactance's for a capacitor and an inductor in RLC circuit?

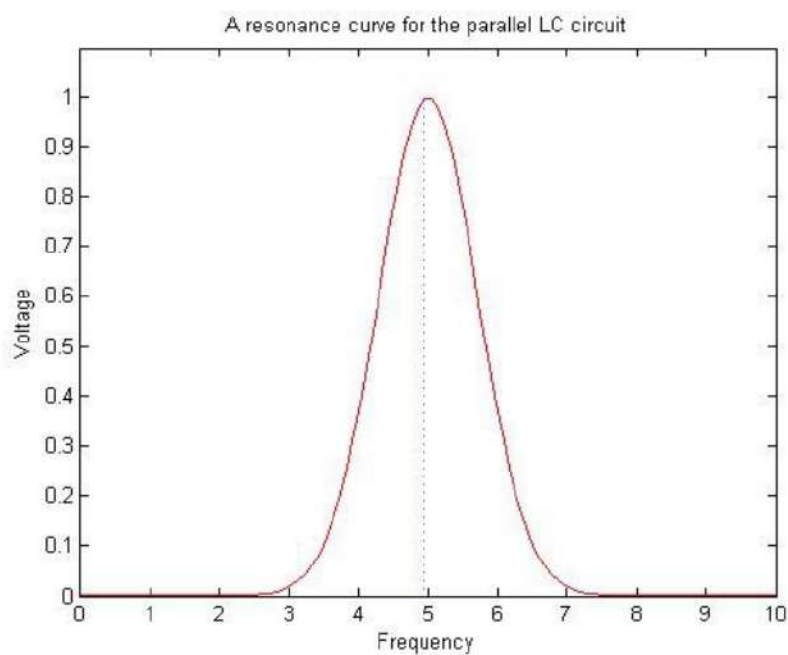2. Determine the resonance frequency and bandwidth from the graph. Find the Q-factor also.



Frequency: _____ KHz

Bandwidth: _____ KHz

Q-Factor: _____